

Introduction to Analyzing Noise in Photodiode Amplifiers

Presented By: S.E Nickols for the staff of Gen-Probe

Nick's Background.

- **Experience:** Over 20 years of electronics/systems design , design analysis, design verification , product certification, manufacturing transfer, and vendor management. Have recent experience with medical device development. Have had involvement with design control, risk management and regulatory issues. (class II and III)
- **Industries:** Scientific, Semiconductor, and Medical.
- **Interests:** Projects requiring a multidisciplinary approach to solve a customer's problem.
- **Approach:** Team player. Quality Oriented. Process oriented. Customer oriented.
- **What I Bring to table:** Aside from technical skill and experience, “hind sight”, a can do attitude, flexible, strong adaptation skills, open minded, here to make you money.

Presentation Contents

- **Photodiode Review**
- Photo Detector Basics
- Noise Concepts Review
- Photodiode and Amplifier Noise Theory
- Bandwidth and Stability Calculations
- Transimpedance Amplifier Theoretical Noise Calculations
- Transimpedance Amplifier Tina Spice Analysis
- Transimpedance Measurement Example

- References
- Appendix



Photodiode Review

Introduction


- Photodiodes convert light into current or voltage.

Commonly Used Photodiode types:

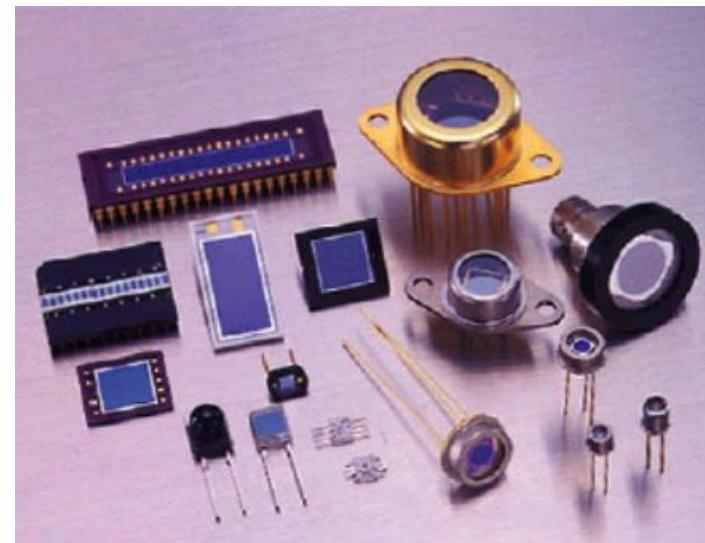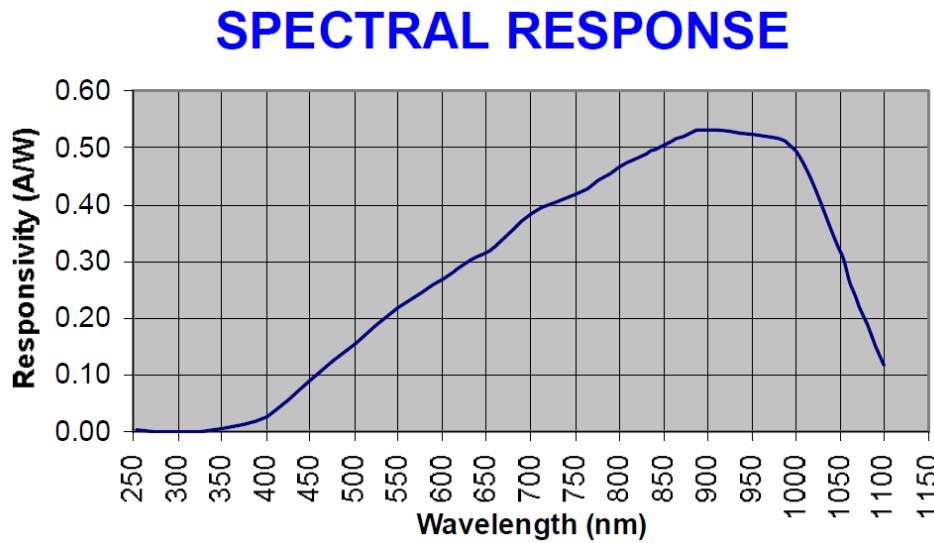- PN photodiode – more wavelength selective (Solar cell)
- PIN photodiode – wide spectral range (less selective) Most widely used.
- APD (Avalanche photodiode) – sensitive to low light, fast




Basic Photodiode Physics

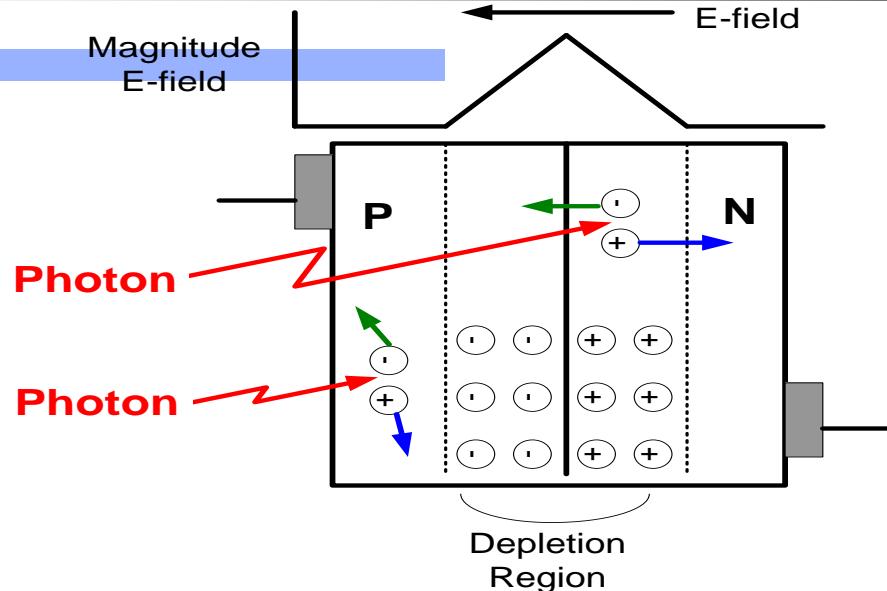

Principle of Operation:


- . - The P-layer material at the active surface and the N material at the substrate form a PN junction which operates as a photoelectric converter.
 - When light strikes a photodiode, the electron within the crystal structure becomes stimulated. If the light energy is greater than the band gap energy E_g , the electrons are pulled up into the conduction band, leaving holes in their place in the valence band.
 - These electron-hole pairs occur throughout the P-layer, depletion layer and N-layer materials. In the depletion layer the electric field accelerates these electrons toward the N-layer and the holes toward the P-layer.
 - This results in a positive charge in the P-layer and a negative charge in the N-layer. If an external circuit is connected between the P- and N-layers, electrons will flow away from the N-layer, and holes will flow away from the P-layer toward the opposite respective electrodes.

Photodiode Circuit Model Basics

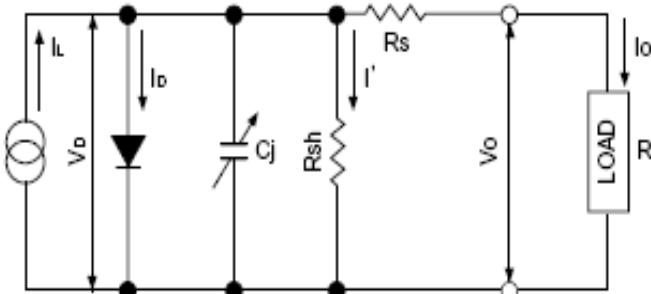

KPDC004EA

Photodiode Equivalent Circuit

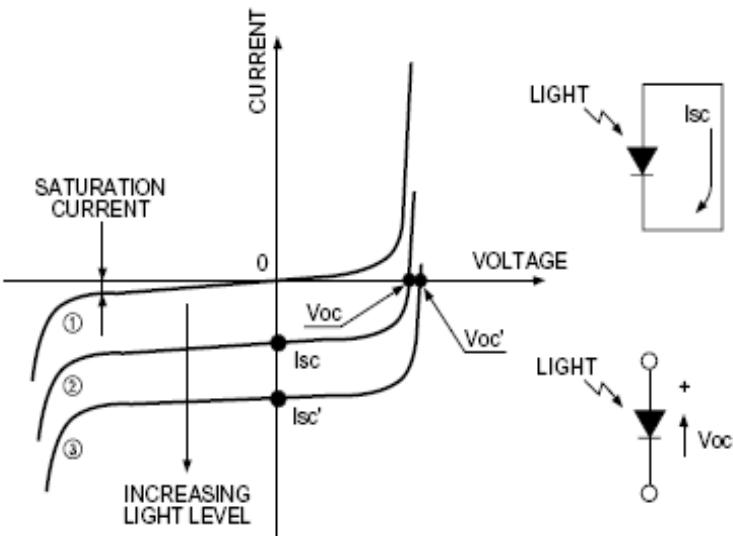

KPDC005EA

Current VS. Voltage Characteristics

$$I_L = r_\phi \phi_e$$

r_ϕ is the diode's flux responsivity

ϕ_e is the radiant flux energy in Watts

I_D : Diode Current

C_j : Junction capacitance

$$C_j = \frac{C_{j0}}{\sqrt{1 + \frac{V_R}{\phi_B}}}$$

C_{j0} is the photodiode capacitance at zero bias

ϕ_B is the built-in voltage of the diode junction

V_R is the reverse bias voltage

R_{sh} : Shunt resistance

R_s : Series resistance


I' : Shunt resistance current

V_D : Diode Voltage

I_o : Output current

V_o : Output voltage

Photodiode Basics Continued

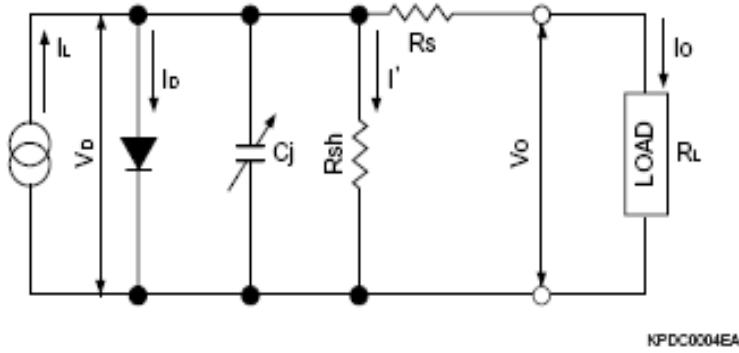

Use left equivalent circuit, the output current is given as :


$$I_o := I_L - I_D - I' = I_L - I_S \left(e^{\frac{eV_D}{kT}} - 1 \right) - I'$$

I_S : Photodiode reverse saturation current

e: electron charge

k: Boltzmann's constant

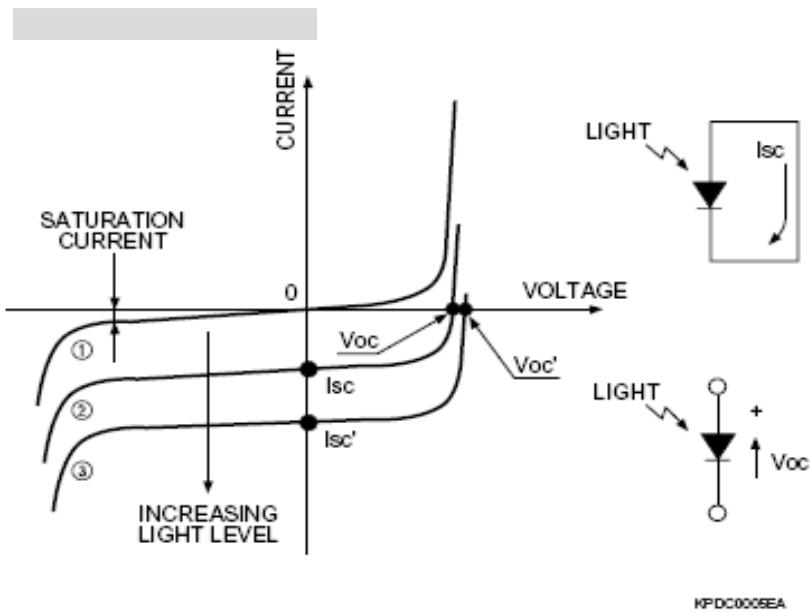T: Absolute temperature of the photodiode



The open circuit voltage V_{oc} is the output voltage when I_o equals 0. Thus V_{oc} becomes:

$$V_{oc} := \frac{kT}{c} \ln \left(\frac{I_L - I'}{I_S} + 1 \right)$$

Current VS. Voltage Characteristics

Photo Diode Properties

Key Properties

The most important properties of photodiodes are:

- The responsivity, i.e., the photocurrent divided by optical power – related to the quantum efficiency, dependent on the wavelength where $h\nu$ is the photon energy, η is the quantum efficiency, and e the elementary charge. For example, a photodiode with 90% quantum efficiency at a wavelength of 800 nm, the responsivity would be $\approx 0.58 \text{ A/W}$. The quantum efficiency of a photodiode is the fraction of the incident (or absorbed) photons which contribute to the photocurrent.
- The active area, i.e., the light-sensitive area
- The maximum allowed photocurrent (usually limited by saturation)
- The dark current (in photoconductive mode, important for the detection of low light levels)
- The speed, i.e. response time, related to the rise and fall time, often influenced by the capacitance.
- Notes:

$$R = \eta \frac{e}{h\nu}$$


Higher photocurrents are actually desirable for suppression of shot noise and thermal noise. Larger active areas (with diameters up to the order of 1 cm) allow for handling of larger beams and for much higher photocurrents, but at the expense of lower speed.

The quantum efficiency of a photodiode can be very high – in some cases more than 95% – but varies significantly with wavelength. Apart from a high internal efficiency, a high quantum efficiency requires the suppression of reflections e.g. with an anti-reflection coating.

Semiconductor Materials

Commonly used photodiode materials are:

- Silicon (Si): low dark current, high speed, good sensitivity between roughly 400 and 1000 nm (best around 800–900 nm).
- Germanium (Ge): high dark current, slow speed due to large parasitic capacity, good sensitivity between roughly 900 and 1600 nm (best around 1400–1500 nm).
- Indium Gallium Arsenide Phosphide (InGaAsP): expensive, low dark current, high speed, good sensitivity roughly between 1000 and 1350 nm (best around 1100–1300 nm).
- Indium Gallium Arsenide (InGaAs): expensive, low dark current, high speed, good sensitivity roughly between 900 and 1700 nm (best around 1300–1600 nm) The indicated wavelength ranges can sometimes be substantially exceeded by models with extended spectral response.

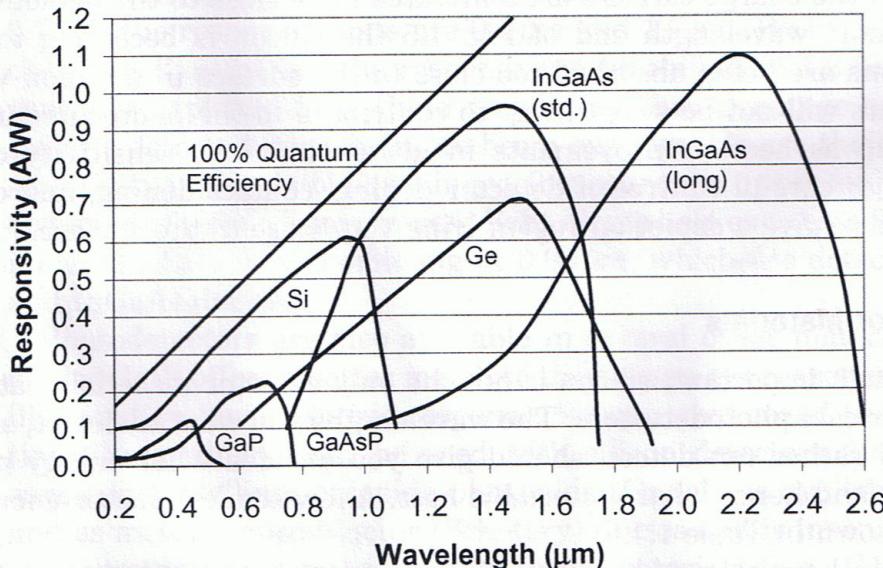


Example Photodiode: “Advanced Photonix” PDB-C158

ABSOLUTE MAXIMUM RATING (TA)= 23°C UNLESS OTHERWISE NOTED

SYMBOL	PARAMETER	MIN	MAX	UNITS
V_{BR}	Reverse Voltage		50	V
T_{STG}	Storage Temperature	-40	+100	°C
T_O	Operating Temperature	-40	+80	°C
T_s	Soldering Temperature*		+260	°C

* 1/16 inch from case for 3 seconds max.

SPECTRAL RESPONSE

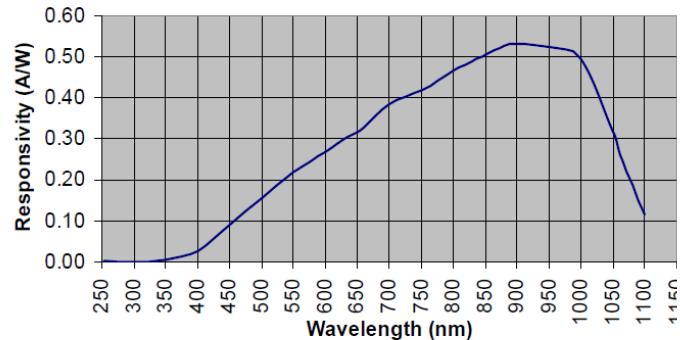

ELECTRO-OPTICAL CHARACTERISTICS RATING (TA)= 23°C UNLESS OTHERWISE NOTED

SYMBOL	CHARACTERISTIC	TEST CONDITIONS	MIN	TYP	MAX	UNITS
I_{SC}	Short Circuit Current	$H = 100 \text{ fc}, 2850 \text{ K}$	100	145		μA
I_D	Dark Current	$V_R = 10 \text{ V}$		2	30	nA
R_{SH}	Shunt Resistance	$V_R = 10 \text{ mV}$	100	150		$M\Omega$
C_J	Junction Capacitance	$V_R = 10 \text{ V}, f = 1 \text{ MHz}$		10	25	pF
λ range	Spectral Application Range	Spot Scan	400		1100	nm
V_{BR}	Breakdown Voltage	$I = 10 \mu\text{A}$	30	75		V
NEP	Noise Equivalent Power	$V_R = 10\text{V} @ \lambda = \text{Peak}$		4.4×10^{-14}		$\text{W}/\sqrt{\text{Hz}}$
t_r	Response Time	$RL = 1\text{K}\Omega, V_R = 10 \text{ V}$		50		nS

**Response time of 10% to 90% is specified at 660nm wavelength light.

C_j is not specified at V_r=0V.

Calling the manufacturer for this information, C_j=70pF for V_r=0V

PIN Diode Structure

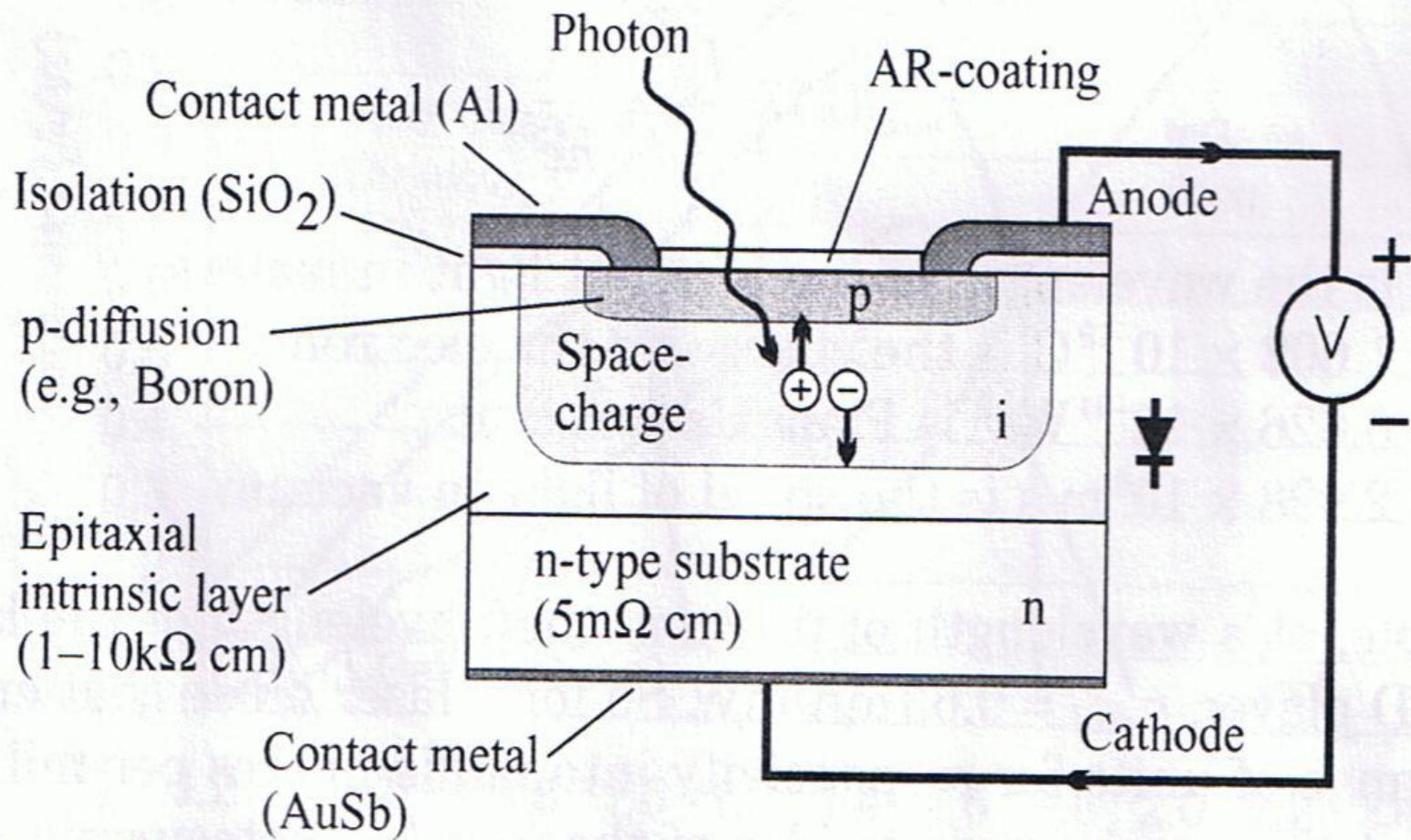


Photo Detector Basics

Basic Photodetector Circuit

Simple?

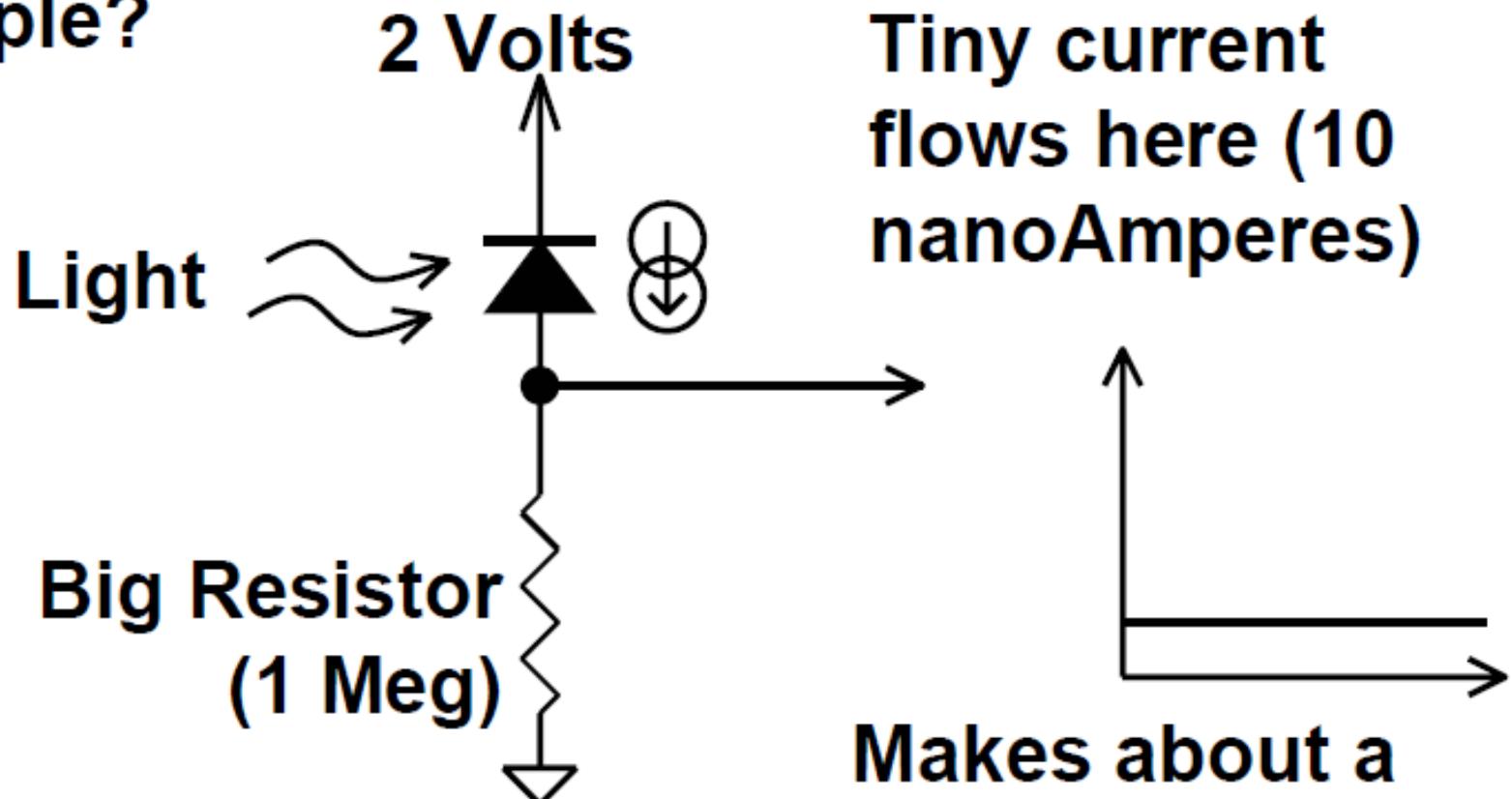


Photo Voltaic Mode Amplifier

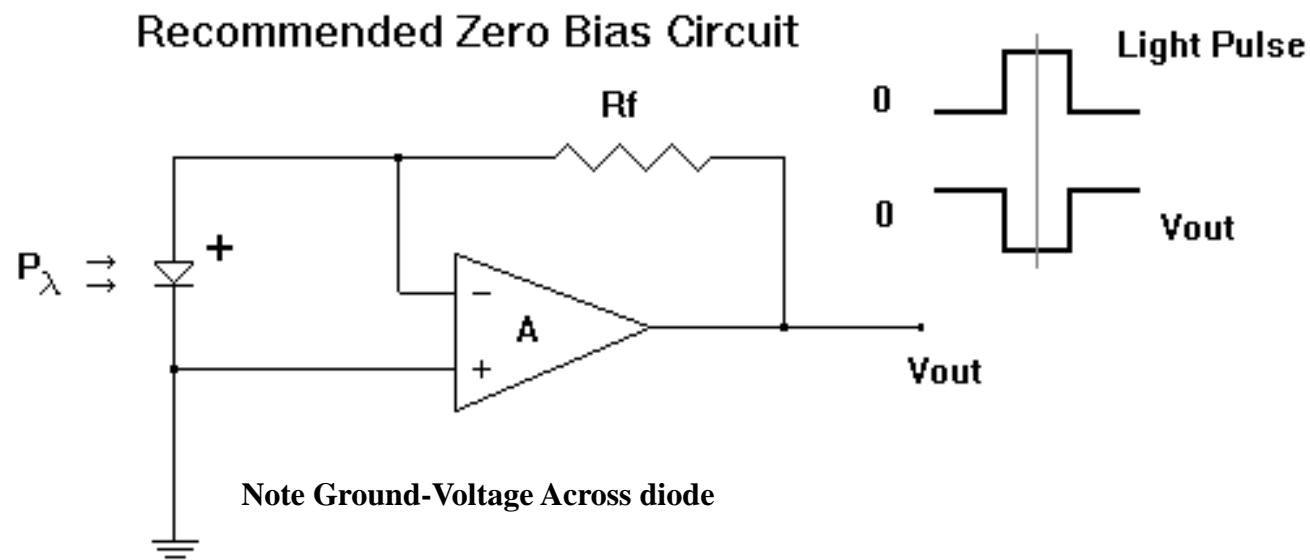


Photo Voltaic Mode Amplifier

Use Photovoltaic Mode:


- Where precision is more important than speed.

The lack of dark current removes an entire error term. The lower noise makes smaller measurements possible. The linear output makes calculations trivial.


Photo Conductive Mode



Positive Bias Circuit

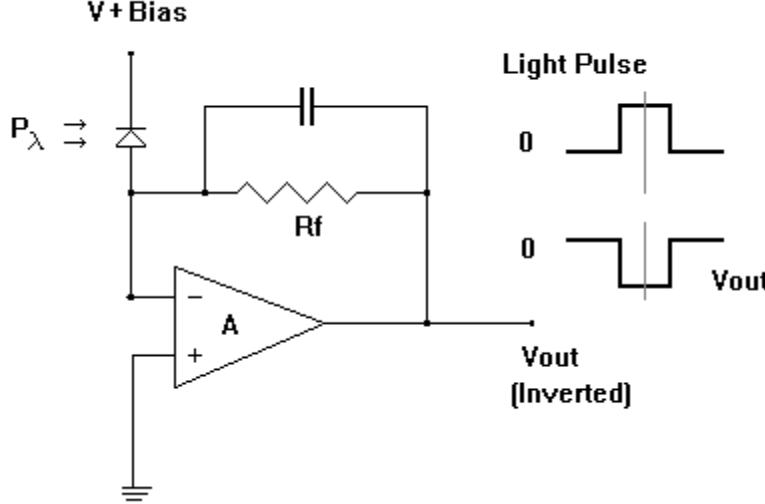

Negative Bias Circuit

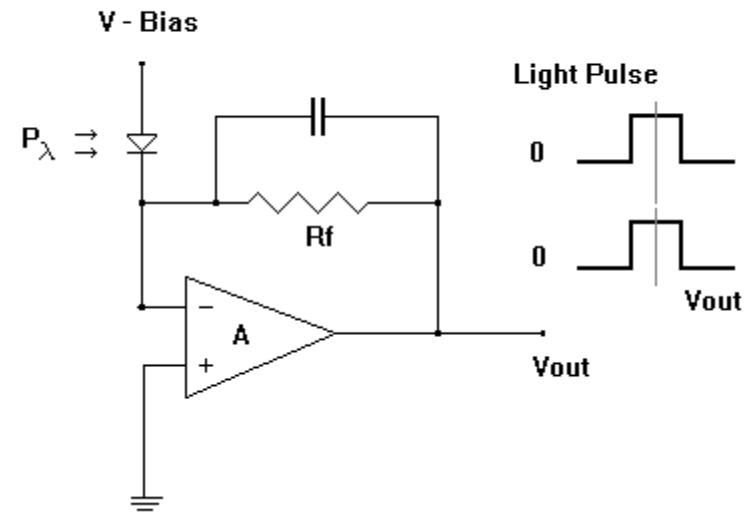

$\pm 10V$, there is voltage across the diode.

Photo Conductive Mode Amplifier



Use Photoconductive Mode:





- Where speed is more important than precision.
The voltage across the diode lowers its capacitance. This allows faster amplifiers:
- Less capacitance allows a faster amplifier while maintaining stability.

Noise Review




Intrinsic Noise

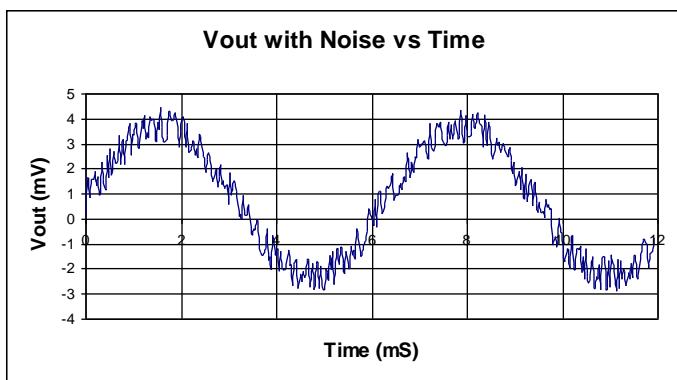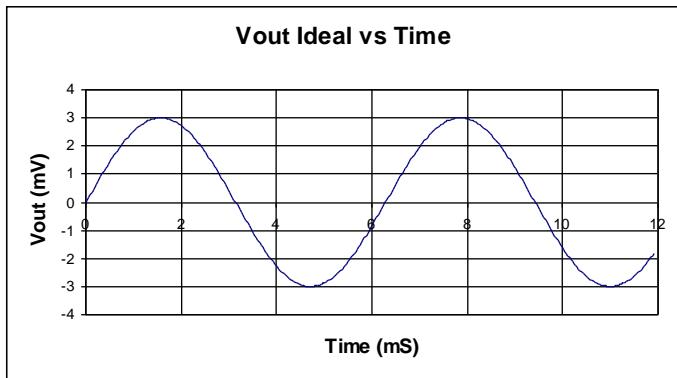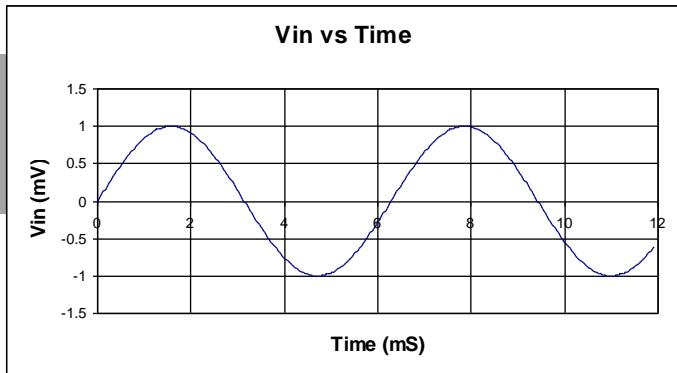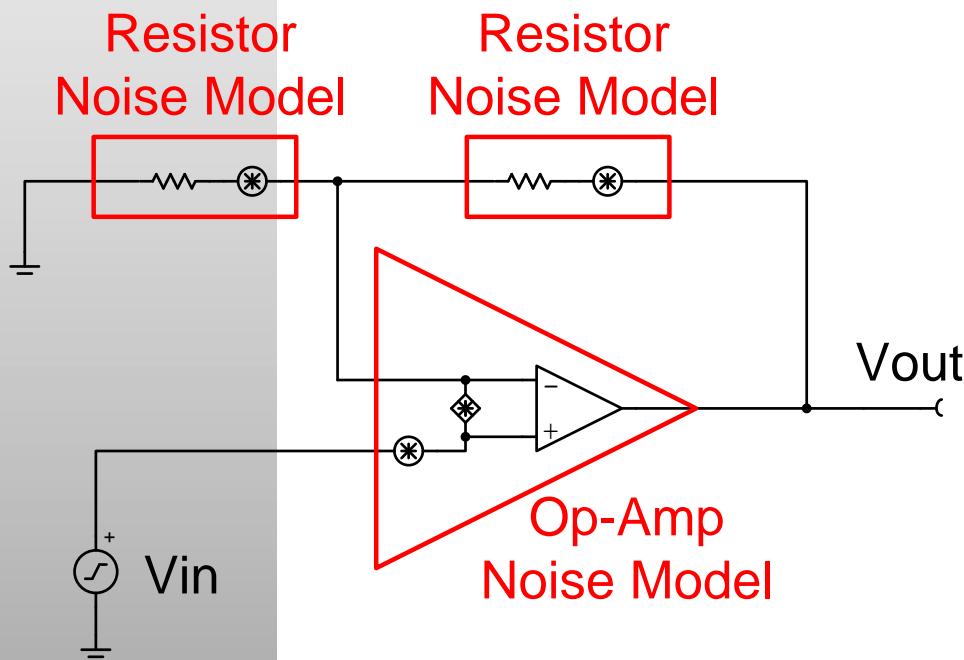- Error Source
- Generated by circuit itself (not pickup)
- Calculate, Simulate, and Measure





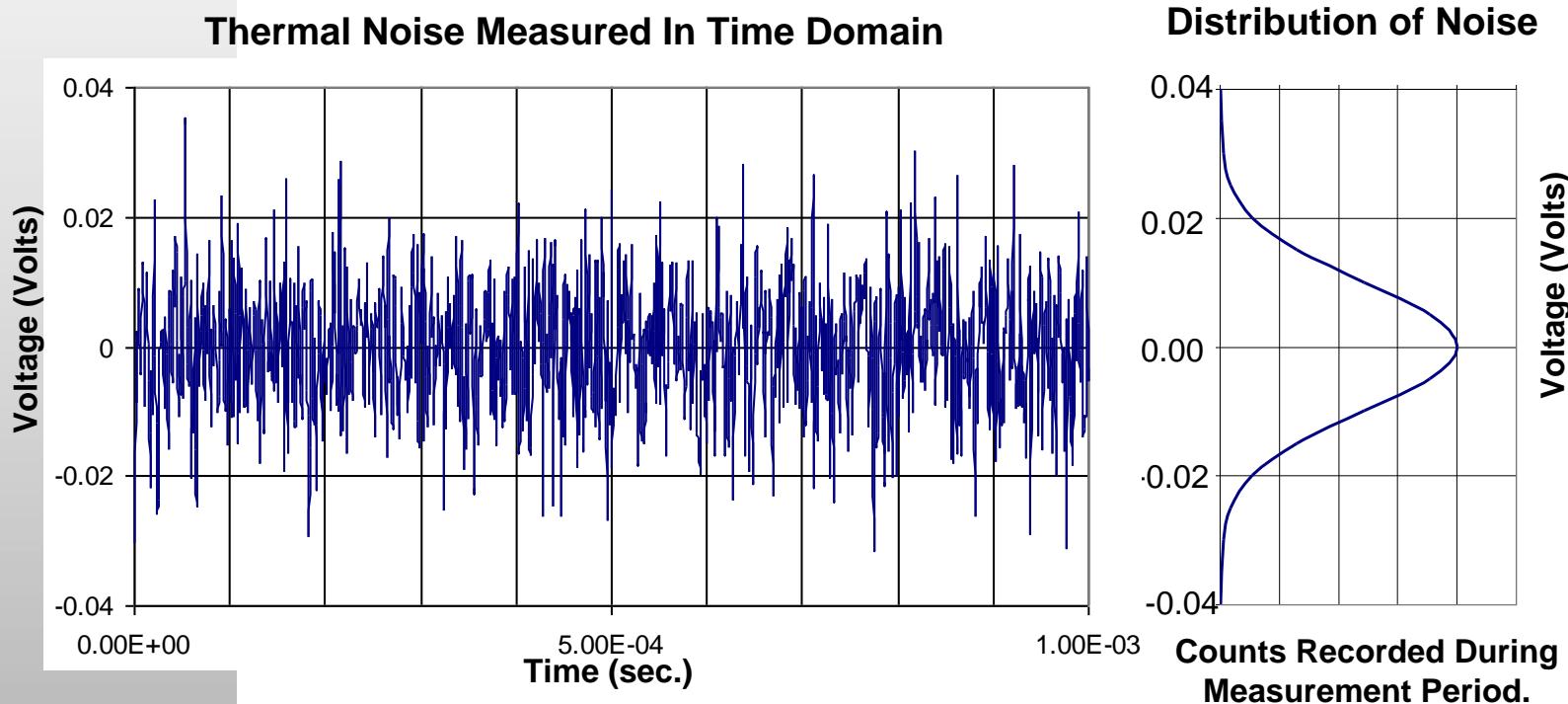Time Domain – White noise normal distribution



What is Spectral Density?


(Noise per unit frequency)

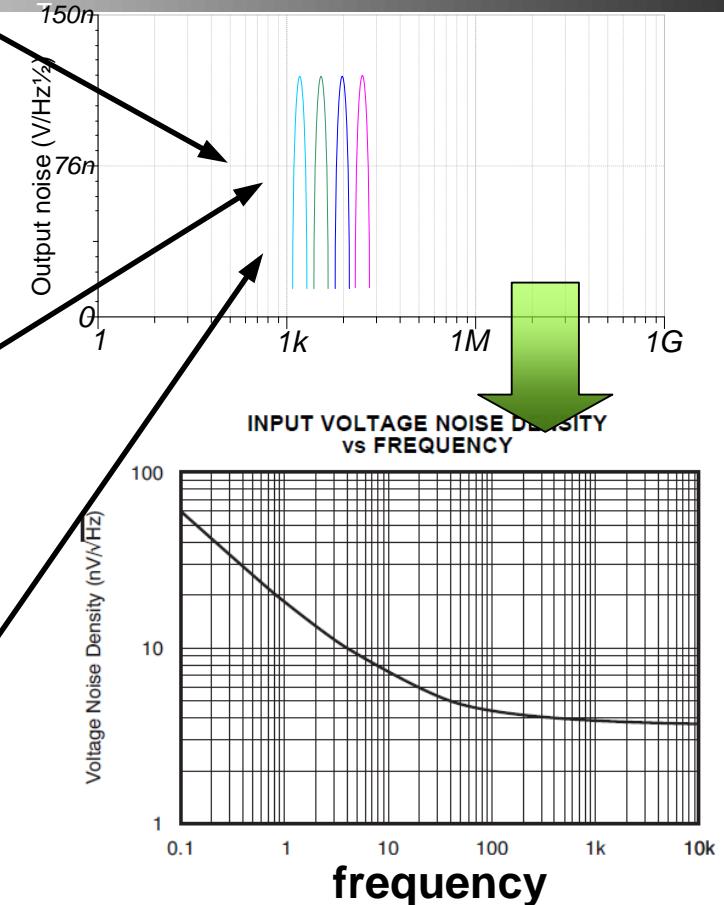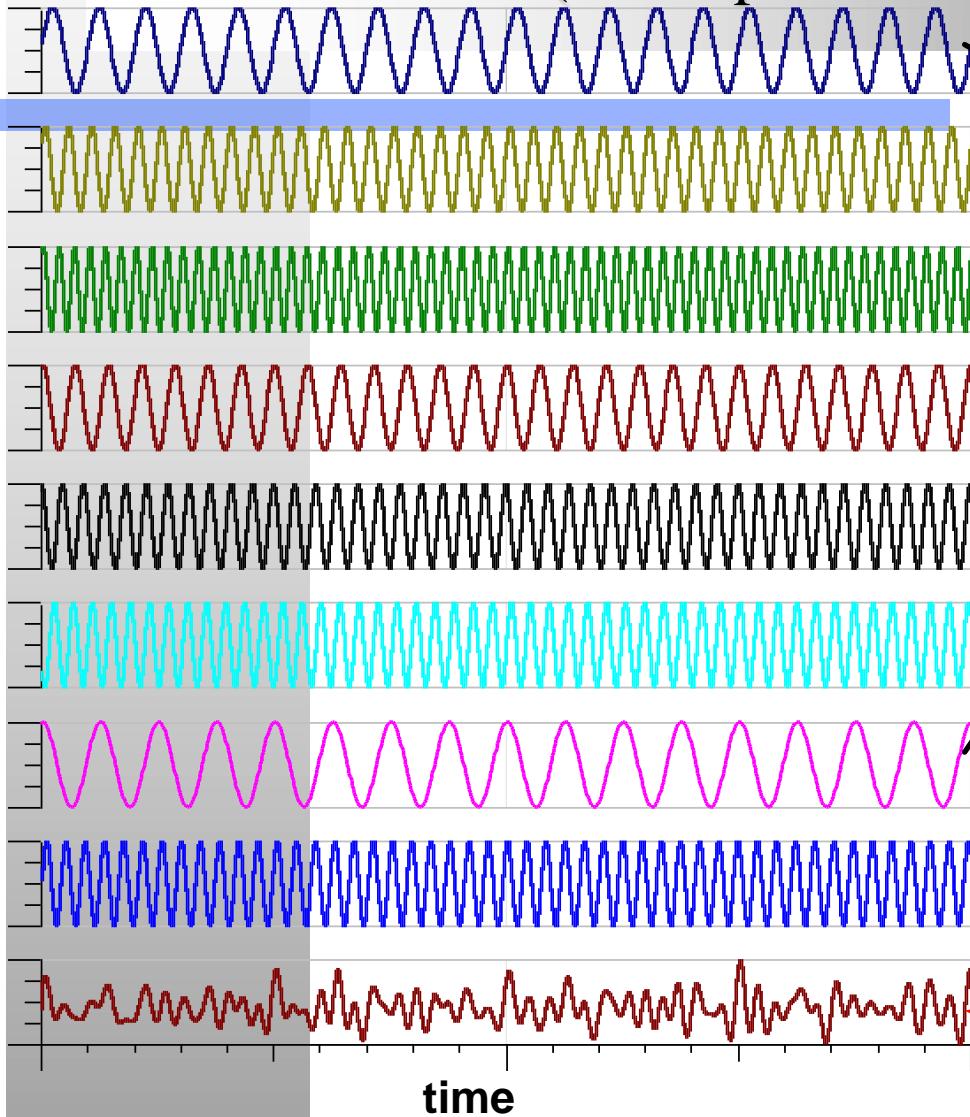

Sum of all frequencies
Random Noise

Convert Spectral Density to RMS

Convert RMS to Peak-to-Peak

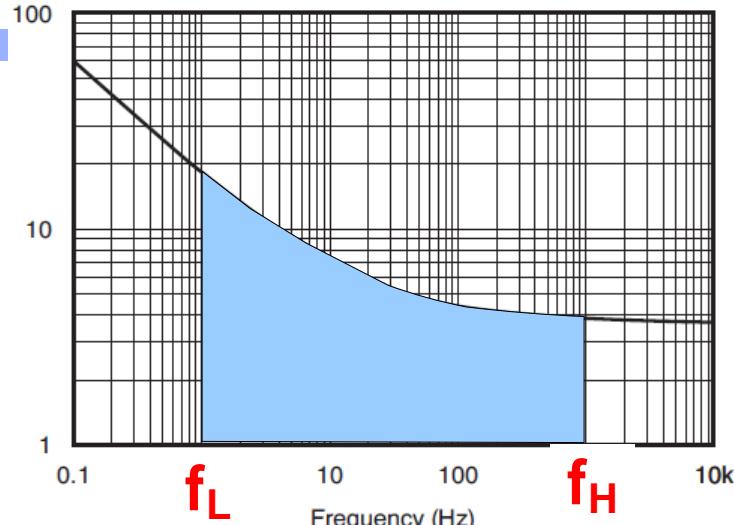


A diagram showing the calculation of the root mean square (RMS) voltage. A grey vertical bar represents the voltage e_n over a period of time. A green arrow points down from the top of the bar to its center, indicating the average value. Below the bar is the equation:

$$\sqrt{\int_{f_L}^{f_H} e_n^2 df} = E_{rms}$$

A green arrow points from the RMS equation to the right, leading to the conversion factor:


$$6 \cdot E_{rms} = E_{pp}$$

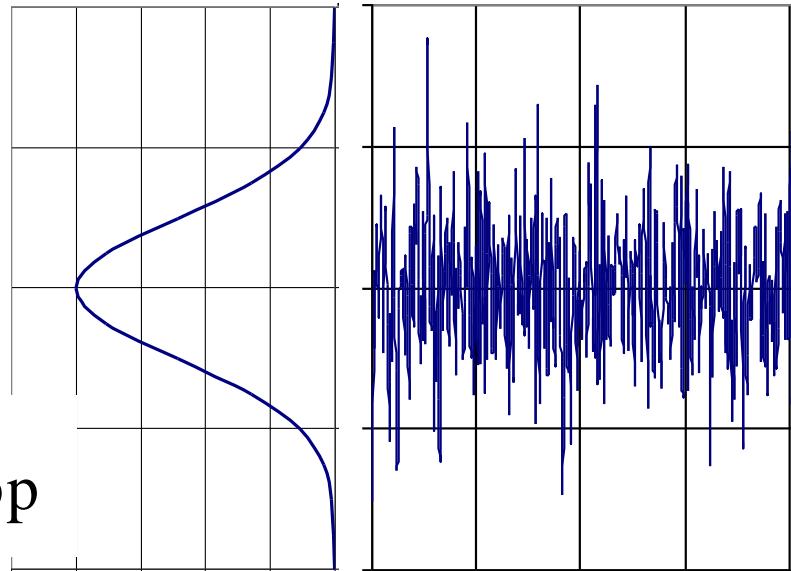

Photodiode vs. Photo Amplifier Noise?


- **Noise is a key parameter in photodiode design**
 - Wide bandwidth (integrate more noise)
 - Low signal levels (noise more critical)
- **Photodiode amplifier noise is more complex**
 - Parasitic capacitance and sensor capacitance
 - Poles and zeros
 - Gain peaking

Sources of Noise

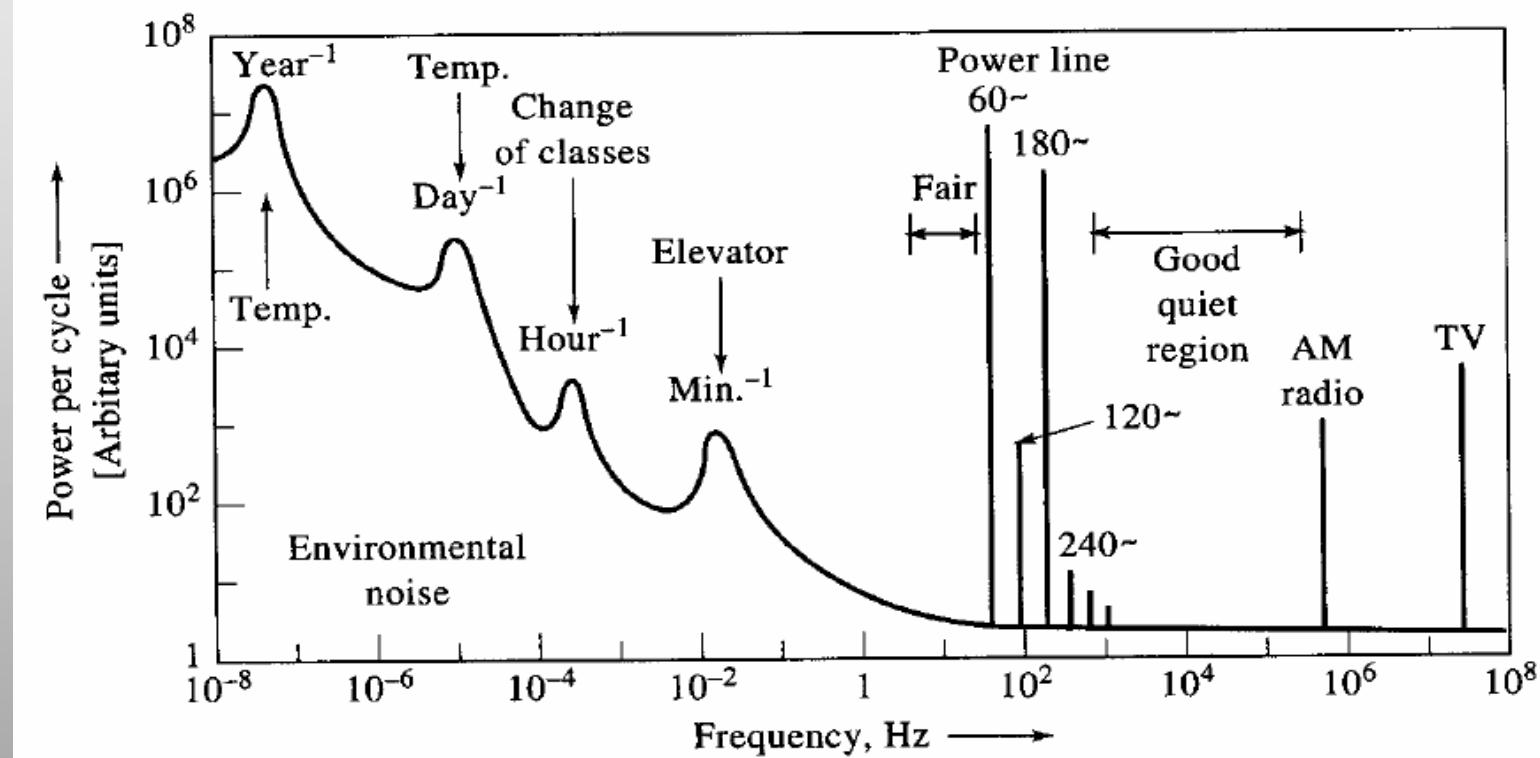

Photodiode Amplifier Noise Theory

Photo-Diode Amp Noise Model

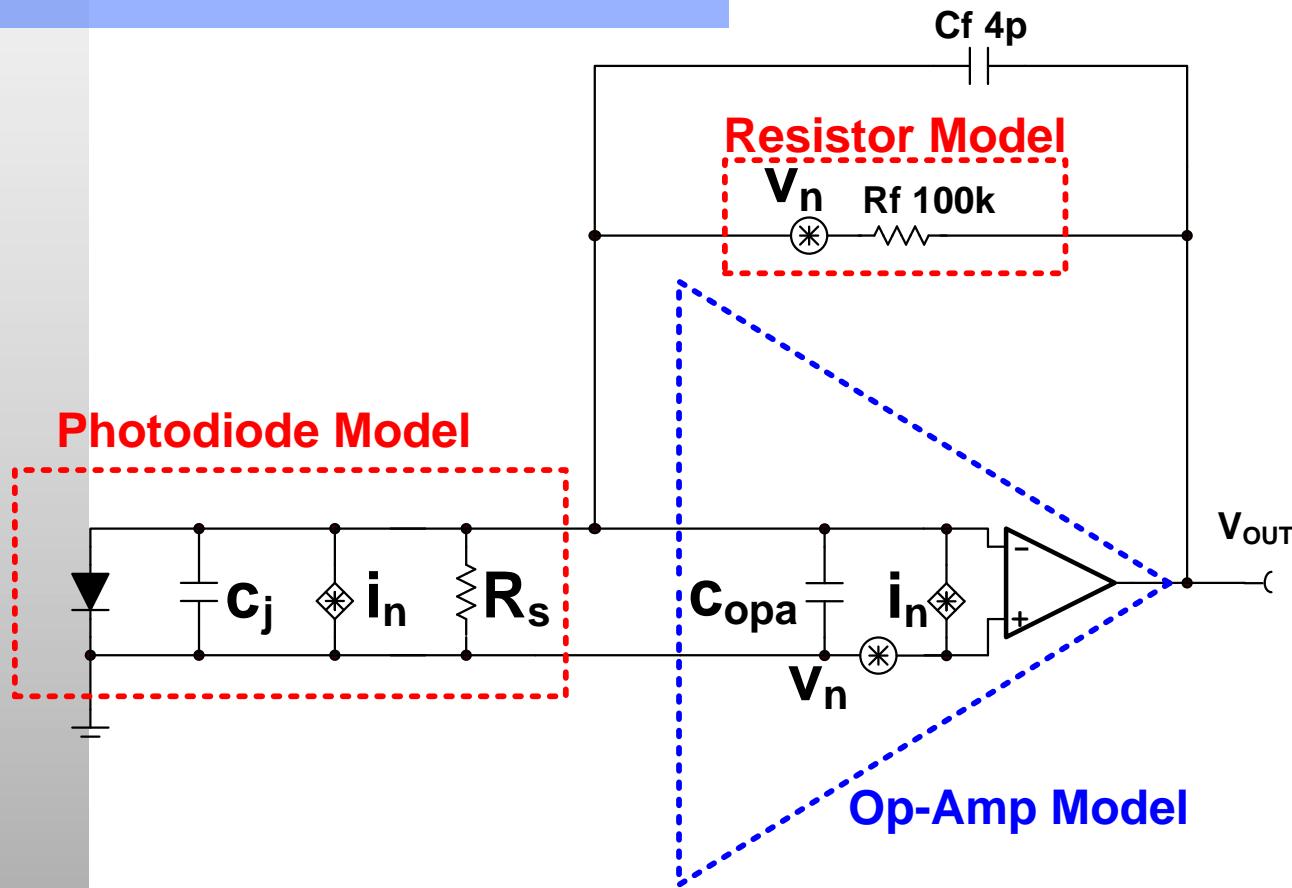

Photodiode Noise

Thermal (Johnson Noise)

k_b Boltzmann constant $1.38 \times 10^{-23} \text{ J/K}$

$$i_j = \sqrt{\frac{4k_b \cdot T_n}{R_{sh}}}$$

q Electron Charge $1.6 \times 10^{-19} \text{ C}$

Shot noise (dark)

T_n Temperature in Kelvin (25C)

$$i_{sD} = \sqrt{2q \cdot I_D}$$

f_p Transconductance bandwidth

Shot noise (w. Light)

$$i_{sL} = \sqrt{2q \cdot I_L}$$


R_{sh} Shunt Resistance in photodiode

Total Diode Current Noise

I_D Dark Current in photodiode

$$i_n = \sqrt{i_j^2 + i_{sD}^2 + i_{sL}^2}$$

I_L Photo current in photodiode


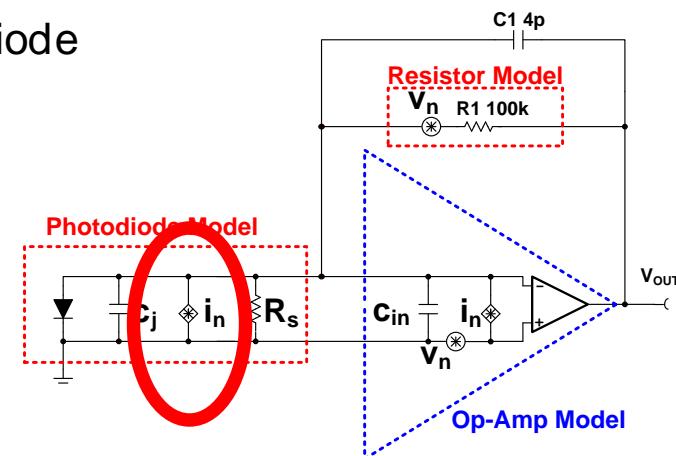


Noise Gain

Simplify the model to compute Noise Gain

$$\text{Noise_Gain} = \frac{V_{\text{out}}}{V_n}$$

Gain seen by the noise voltage source.

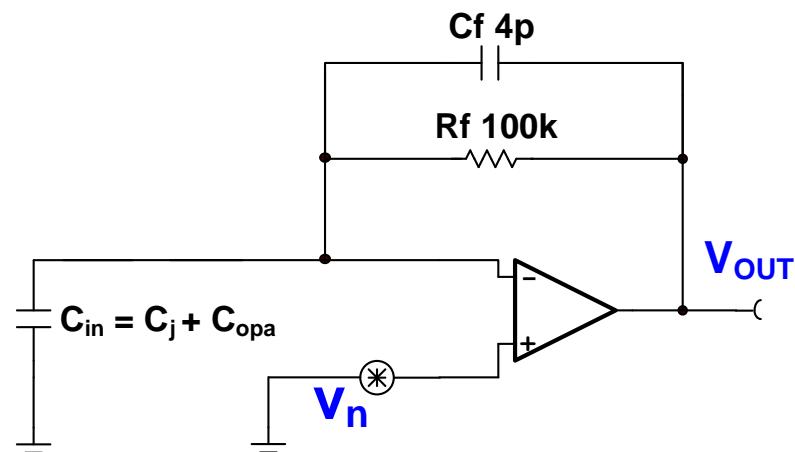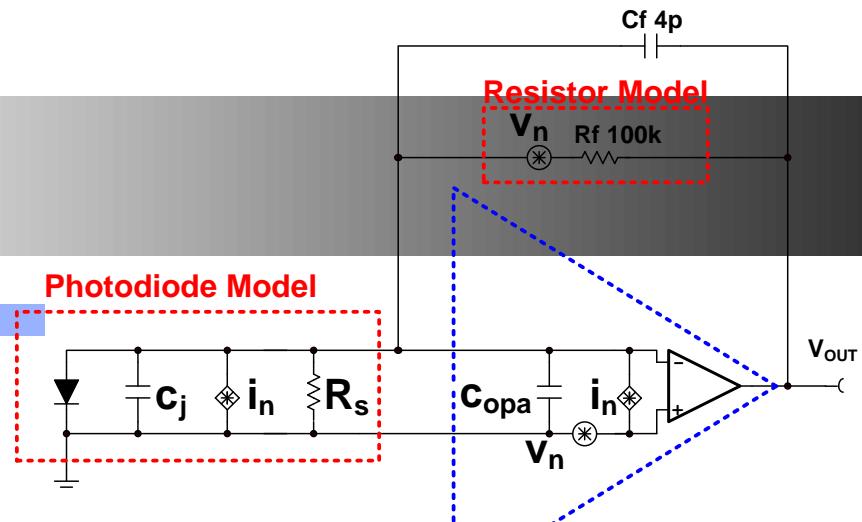

Noise Gain

Nodal Analysis on transimpedance amp

$$\frac{V_n}{\frac{1}{s \cdot C_{in}}} + \frac{(V_n - V_{out})}{R_f} + \frac{V_n - V_{out}}{\frac{1}{s \cdot C_f}} = 0$$

Solve for noise gain V_{out} / V_n



$$\frac{V_{out}}{V_n} = \frac{R_f \cdot (C_f + C_{in}) \cdot s + 1}{C_f \cdot R_f \cdot s + 1}$$

The numerator contains a **Zero**

$$f_z = \frac{1}{2\pi R_f (C_f + C_{in})}$$

The denominator contains a **Pole**

$$f_p = \frac{1}{2\pi R_f C_f}$$

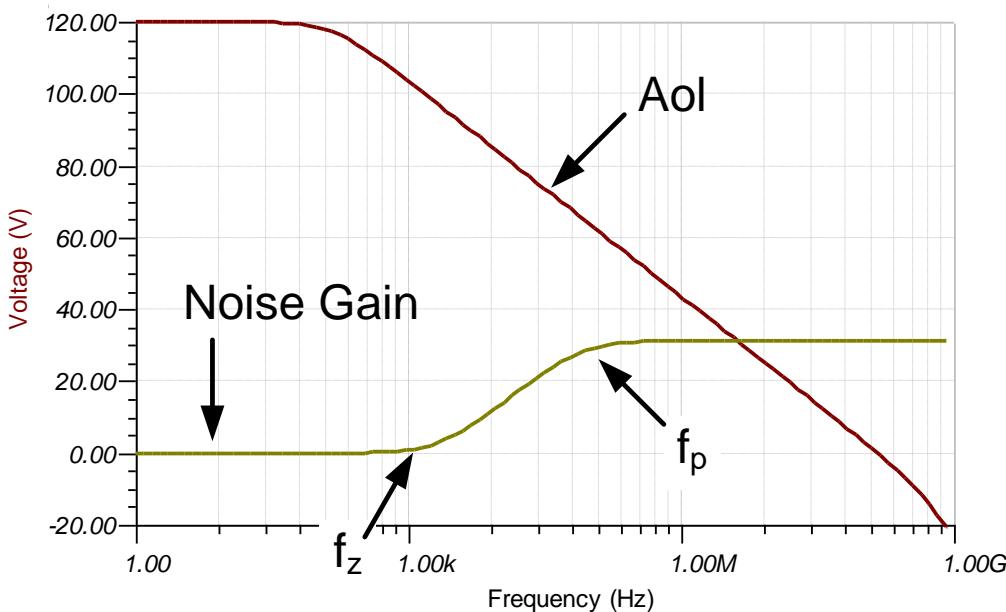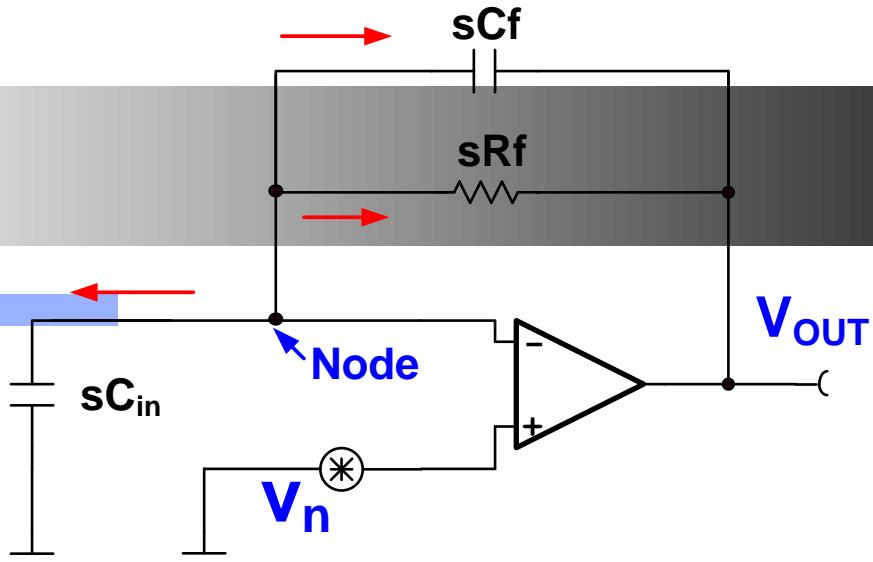

Noise Gain

$$f_i = \frac{C_f}{C_i + C_f} \cdot f_c$$

Intersection of the noise gain curve with the AOL Curve

f_c


Unity Gain Bandwidth from
Op-Amp Data Sheet

$$GPM = 1 + \frac{C_{in}}{C_f}$$

Gain Peak Magnitude




Gain Peak
Magnitude

$1 + C_{in} / C_f$

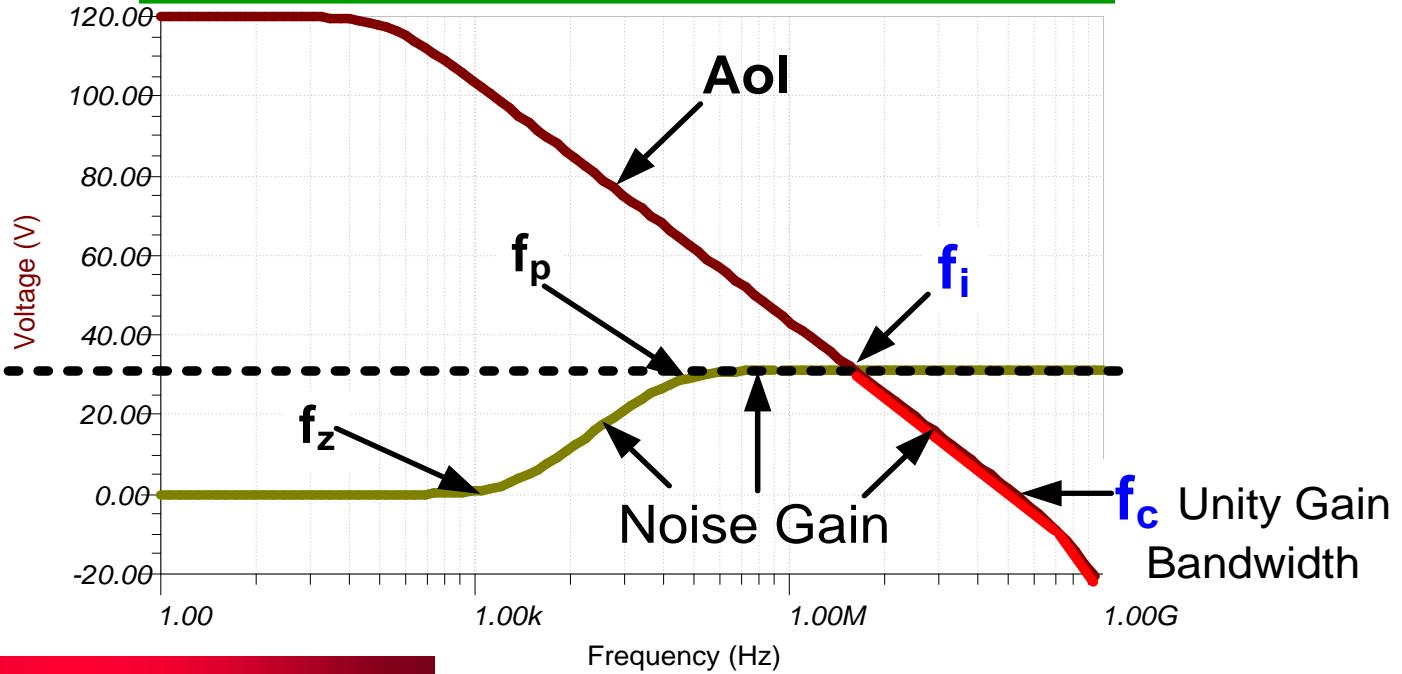


Noise Gain

Op-Amp
Voltage Noise
(Data Sheet)

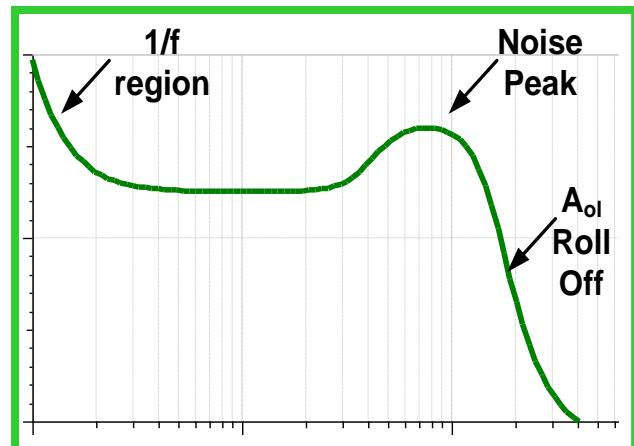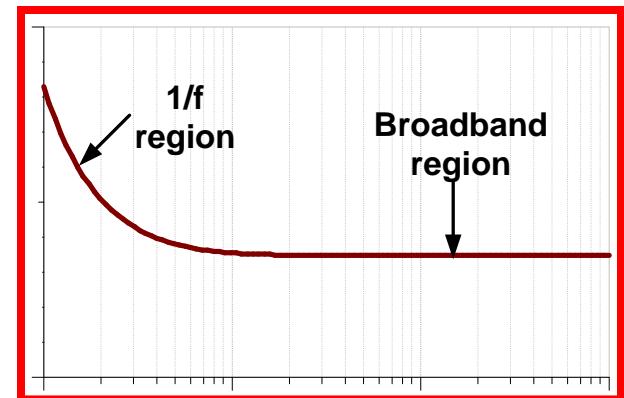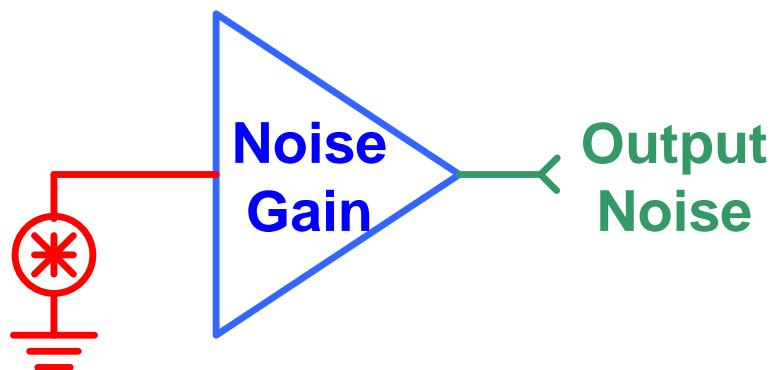

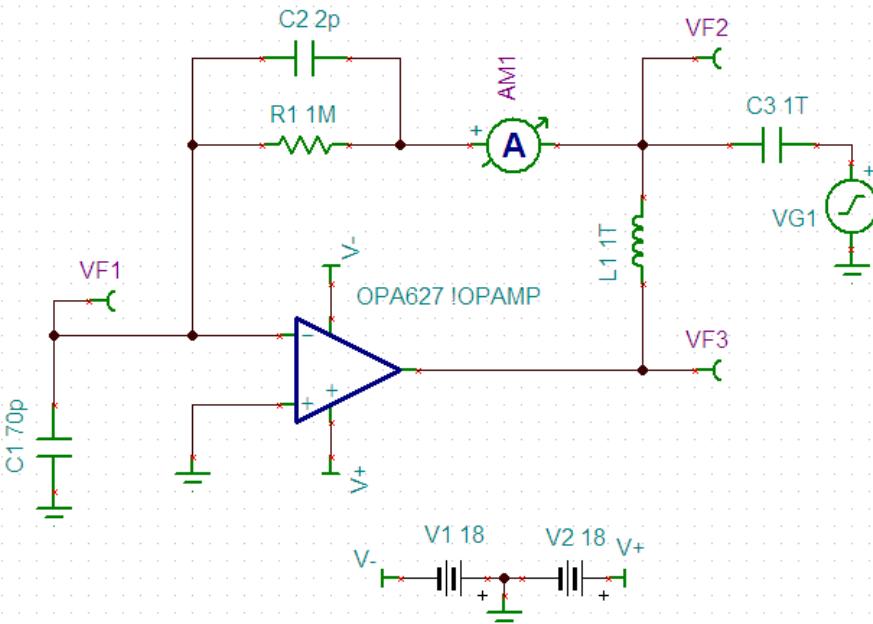Simulating Noise Gain and Noise Bandwidth




$$A_{ol} = \frac{VF_3}{VF_1}$$

$$\text{Noise_Gain} = \frac{1}{\beta} = \frac{VF_2}{VF_1}$$


$$I_{\text{to_V_Gain}} = \frac{VF_3}{AM_1}$$

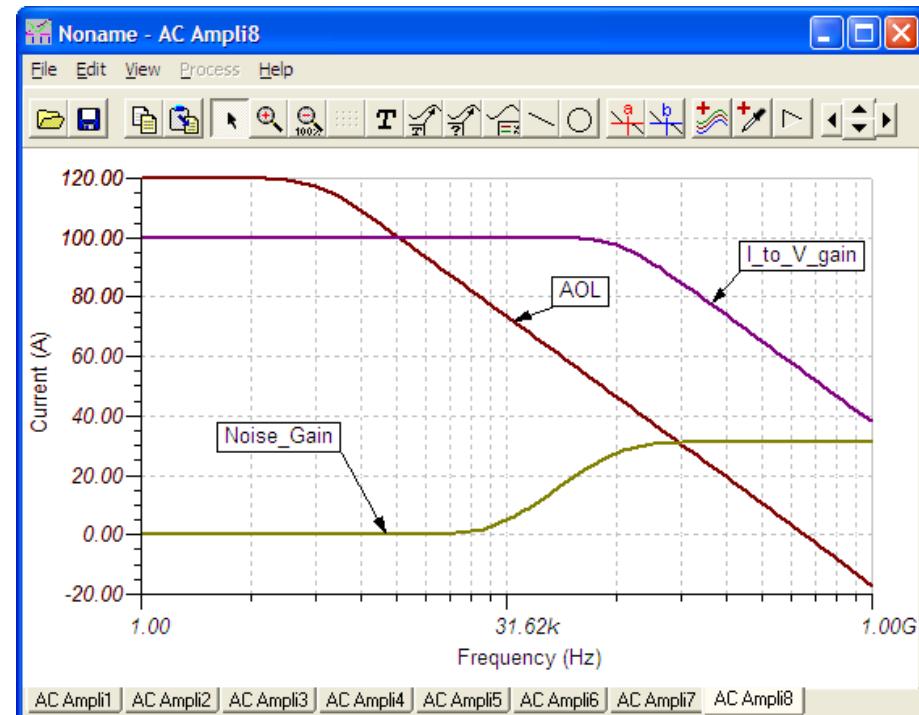- Break the loop to measure AOL, 1/B, and I to V Gain



Voltage Noise eni , eno and Eno
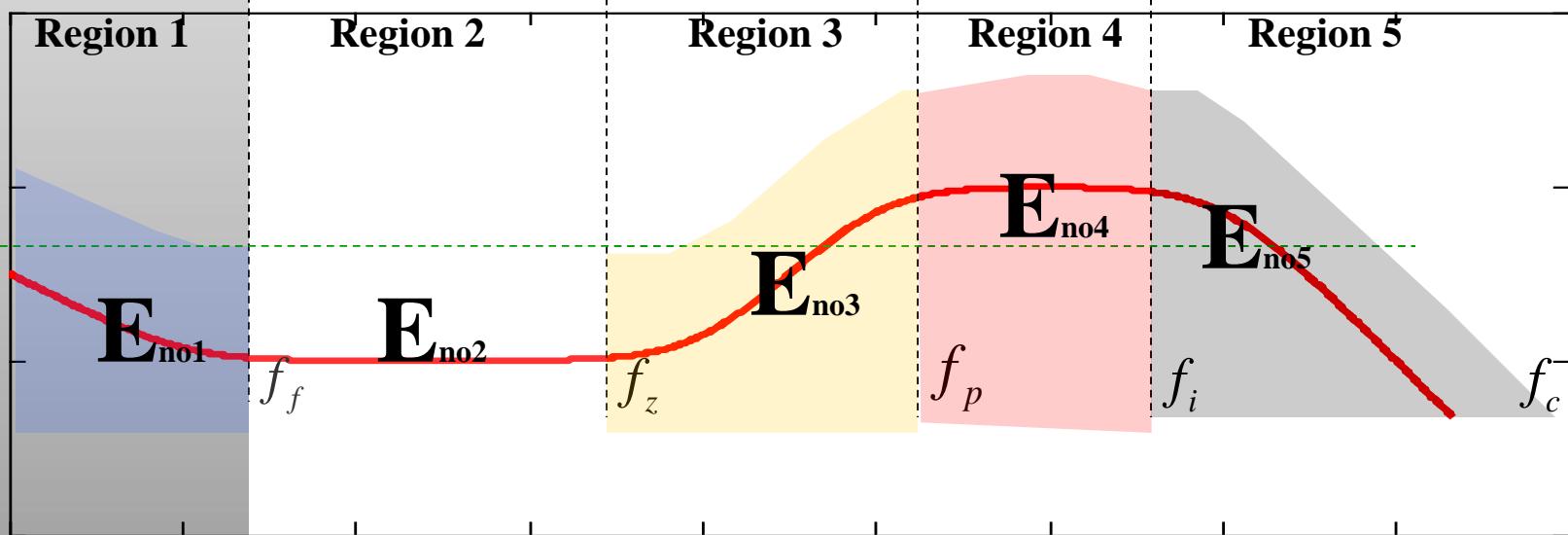
$$e_{no} = A_n \cdot e_{ni} = \frac{\left(1 + \frac{s}{\omega_z}\right) \cdot \sqrt{1 + \frac{\omega_f}{s}}}{\left(1 + \frac{s}{\omega_p}\right) \cdot \left(1 + \frac{s}{\omega_i}\right)}$$



Voltage Noise e_{ni} , e_{no} and E_{no}

Region 1 noise:

$$E_{noe1}^2 = \int_{f_L}^{f_f} \frac{e_{nif}^2 \cdot f_f}{f} d_f = e_{nif}^2 f_f \ln \frac{f_f}{f_L}$$

Region 2 noise:

$$E_{noe2}^2 = \int_{f_f}^{f_z} e_{nif}^2 d_f = e_{nif}^2 (f_z - f_f)$$

Region 3 noise:

$$E_{noe3}^2 = \int_{f_z}^{f_p} \frac{e_{nif}^2 \cdot f^2}{f_z^2} d_f = \left(\frac{e_{nif}}{f_z} \right)^2 \frac{f_p^3 - f_z^3}{3}$$

Region 4 noise:

$$E_{noe4}^2 = \int_{f_p}^{f_i} \left(\frac{e_{nif}}{\beta} \right)^2 d_f = \left(e_{nif} \cdot \frac{C_i + C_f}{C_f} \right)^2 (f_i - f_p)$$

Region 5 noise:

$$E_{noe5}^2 = \int_{f_i}^{\infty} \left(\frac{e_{nif} f_c}{f} \right)^2 d_f = \frac{(e_{nif} f_c)^2}{f_i}$$


Total voltage noise:

$$E_{noe}^2 = E_{noe1}^2 + E_{noe2}^2 + E_{noe3}^2 + E_{noe4}^2 + E_{noe5}^2$$

Voltage Noise eni , eno and Eno


e_{no}

Log scale

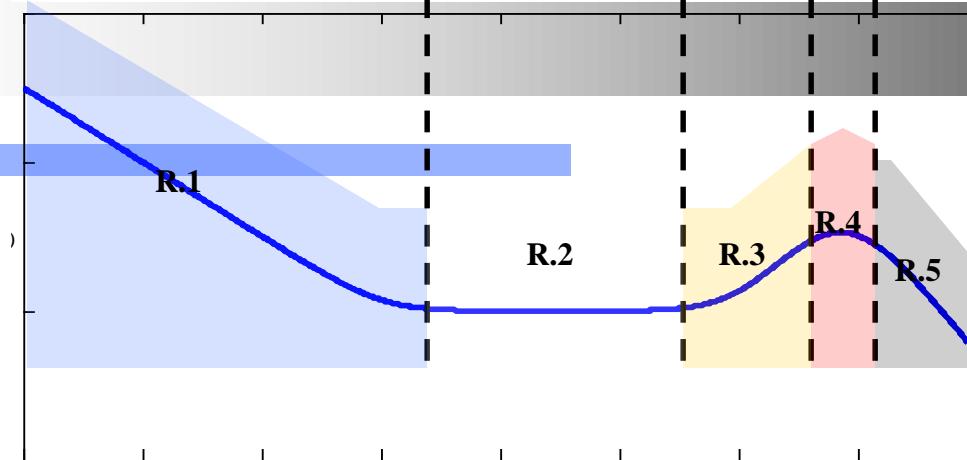

e_{no}


Linear scale

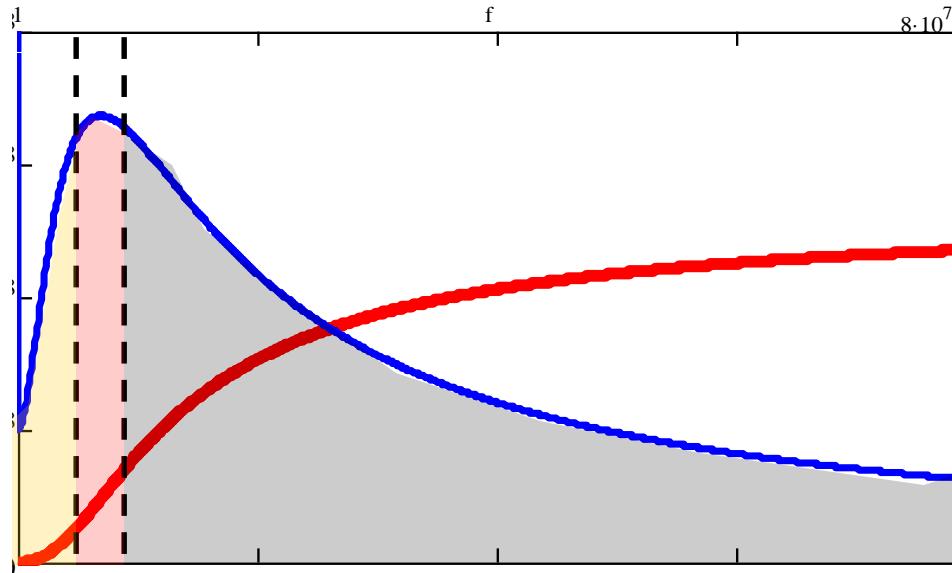

E_{no^2}

Linear scale

Resistor Noise and Current Noise

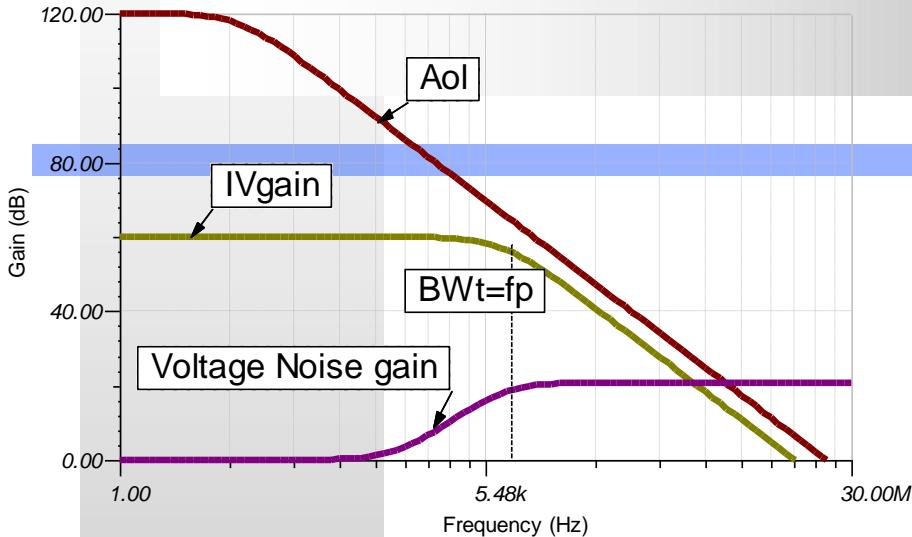


Current noise and resistor noise are limited by the transimpedance (I-V gain) bandwidth

Poles	K _n
1	1.57
2	1.22
3	1.16

$$BW_n = K_n \cdot f_p$$

$$E_{noR} = \sqrt{4K \cdot T \cdot R_f \cdot BW_n}$$

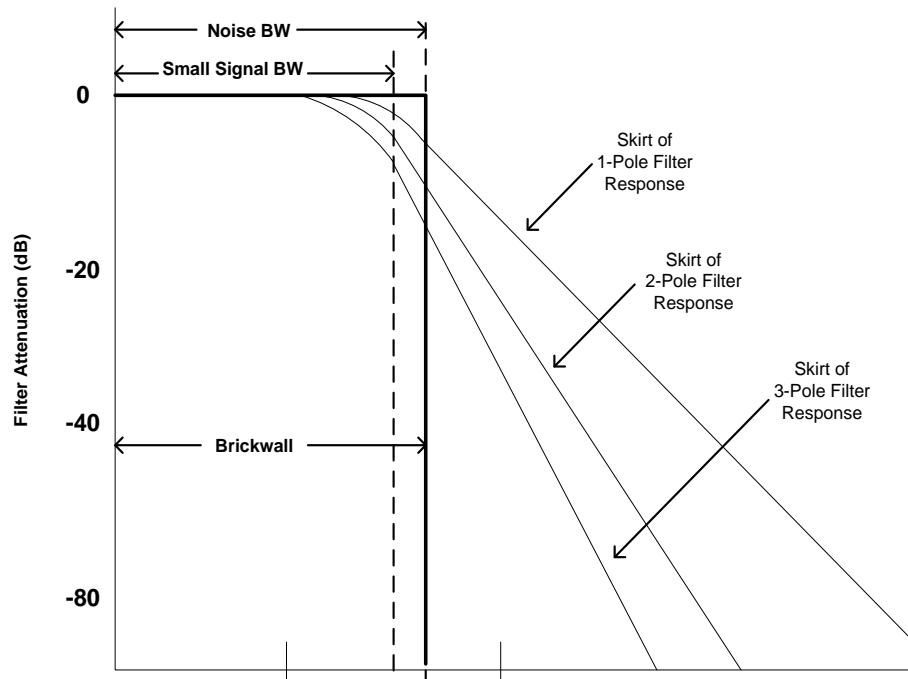
$$E_{no1} = i_{ni} \cdot R_f \cdot BW_n$$



Bandwidth and Stability



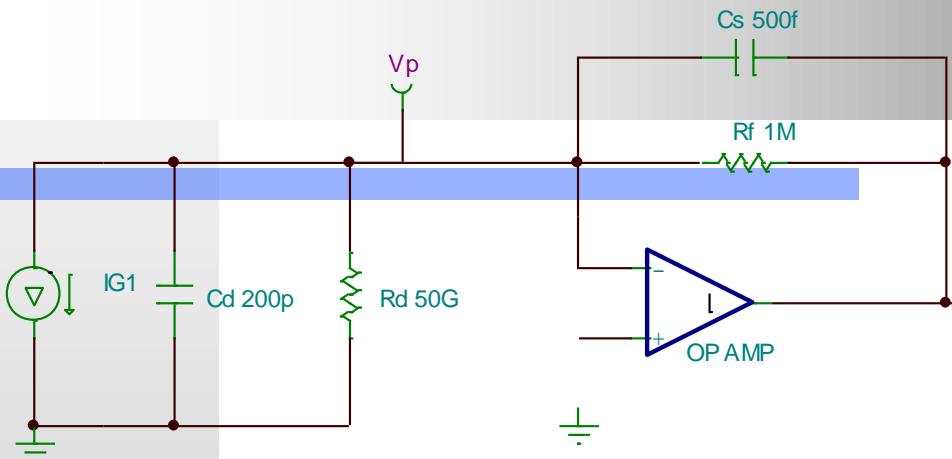
Parasitic Capacitance Limits the Bandwidth




$$f_p = \frac{1}{2\pi R_f \cdot C_f} = 318\text{kHz}$$

• **Max bandwidth with Min C_f**

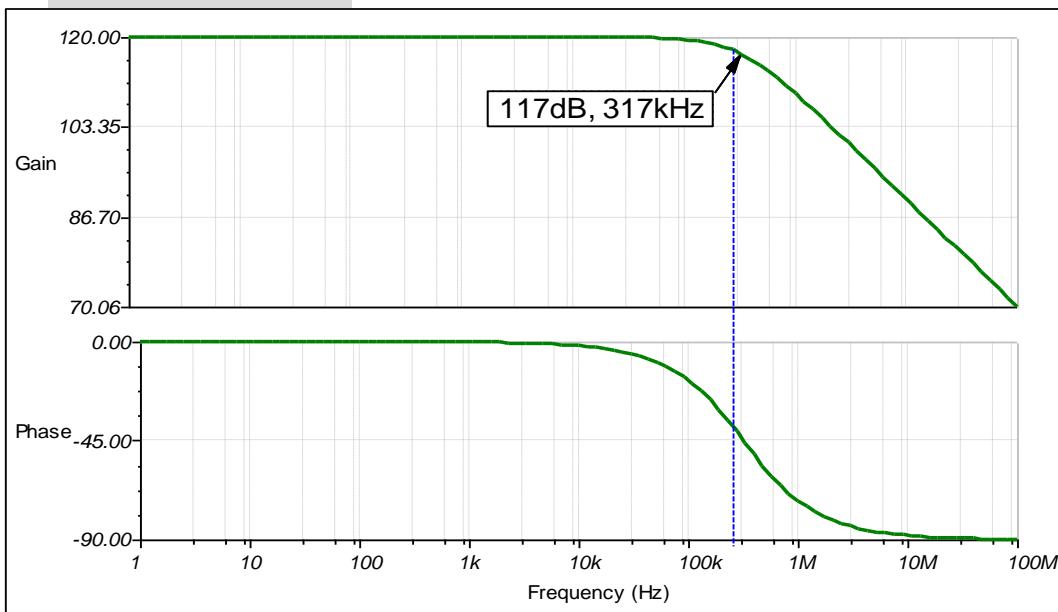
- Low C_f may be unstable
- Wide BW increases noise
- As shown $C_f = C_s$ (stray cap)



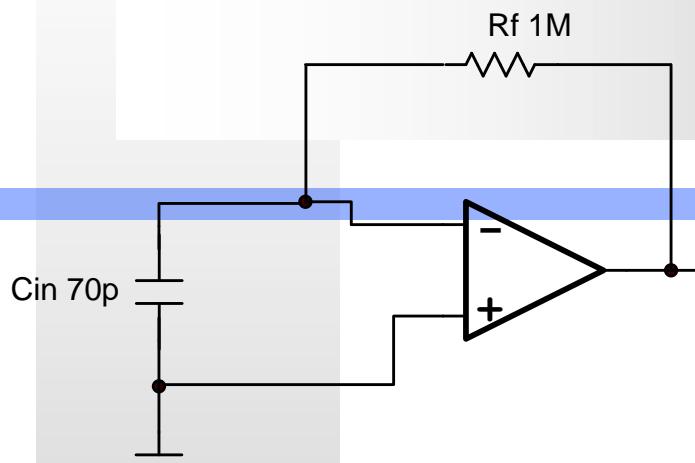
Feedback Capacitance Required for Stability



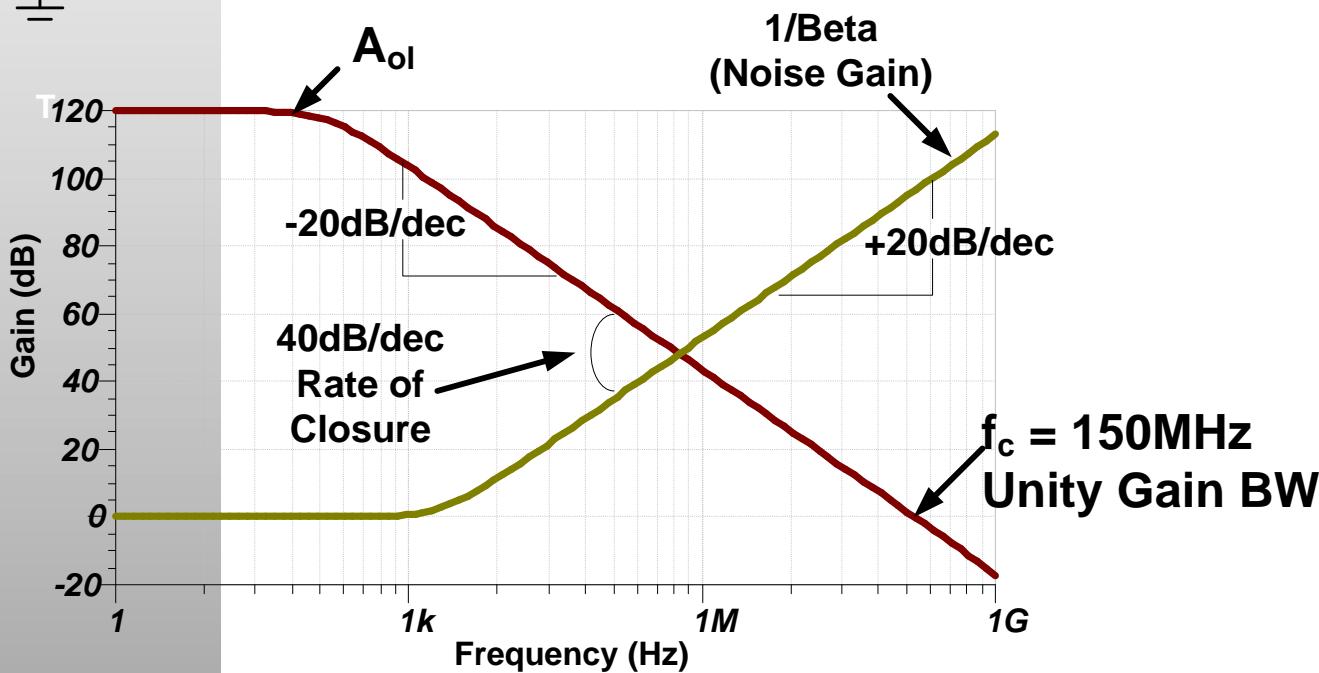
- Noise Gain is key to stability
- Also called 1/Beta (in stability analysis)
- ROC = Rate of Closure
- ROC = (A_{ol} slope) – (1/Beta slope)
- Unstable when ROC > 20dB/decade



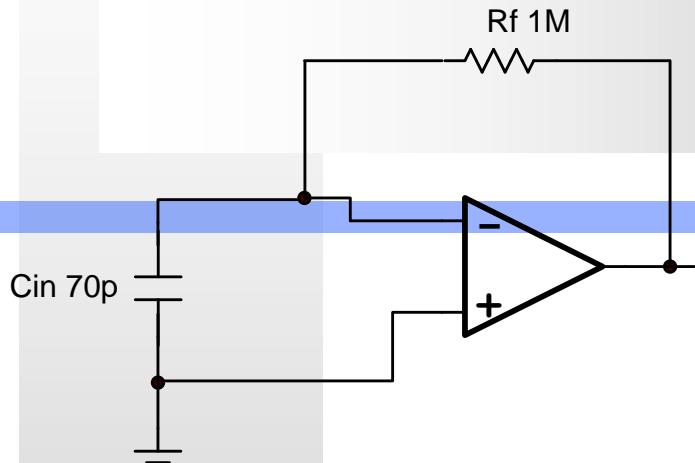
Feedback Capacitance Required for Stability



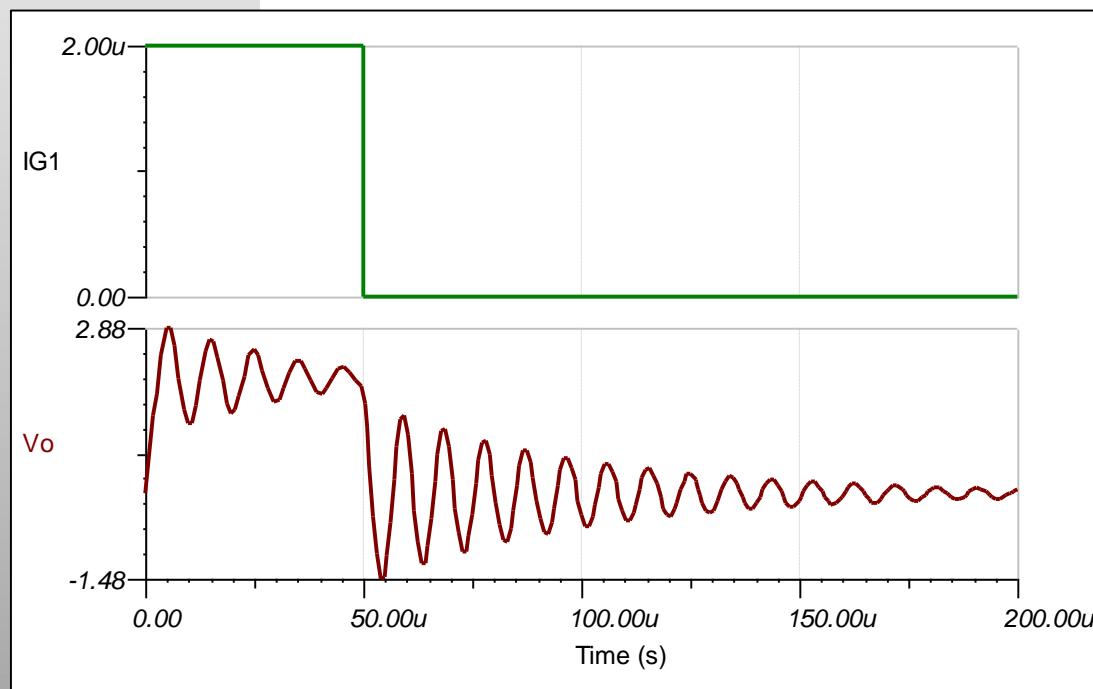Applying a Step Input shows instability at output



Choosing a Minimum Cf for Stability

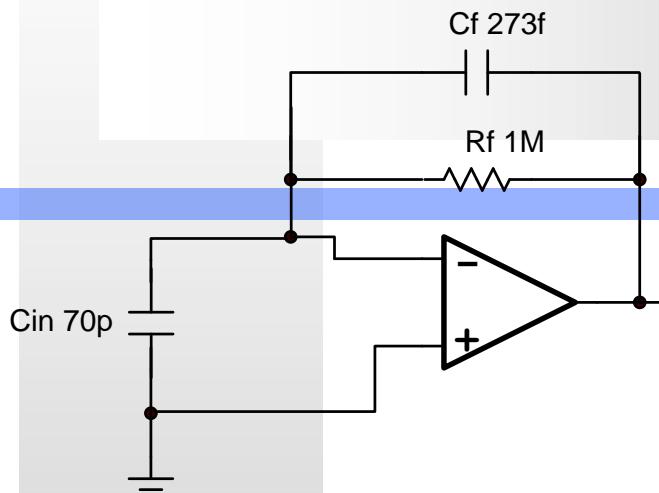

$f_c = 150\text{MHz}$

Op-amp Unity Gain Bandwidth

$C_{in} = 70\text{pF}$

Total input capacitance

$R_f = 1\text{M}\Omega$

Feedback resistance

$$C_f = \sqrt{\frac{C_{in}}{2\pi \cdot R_f \cdot f_c}} = 272.5\text{fF}$$


Simplified equation for minimum feedback cap
Assumes $C_{in} \gg C_f$

$$C_c = \frac{1}{2\pi \cdot R_f \cdot f_c}$$

Intermediate calculation used in more exact formula


$$C_{fe} = \frac{C_c}{2} \cdot \left(1 + \sqrt{1 + \frac{4C_{in}}{C_c}} \right) = 273.1\text{fF}$$

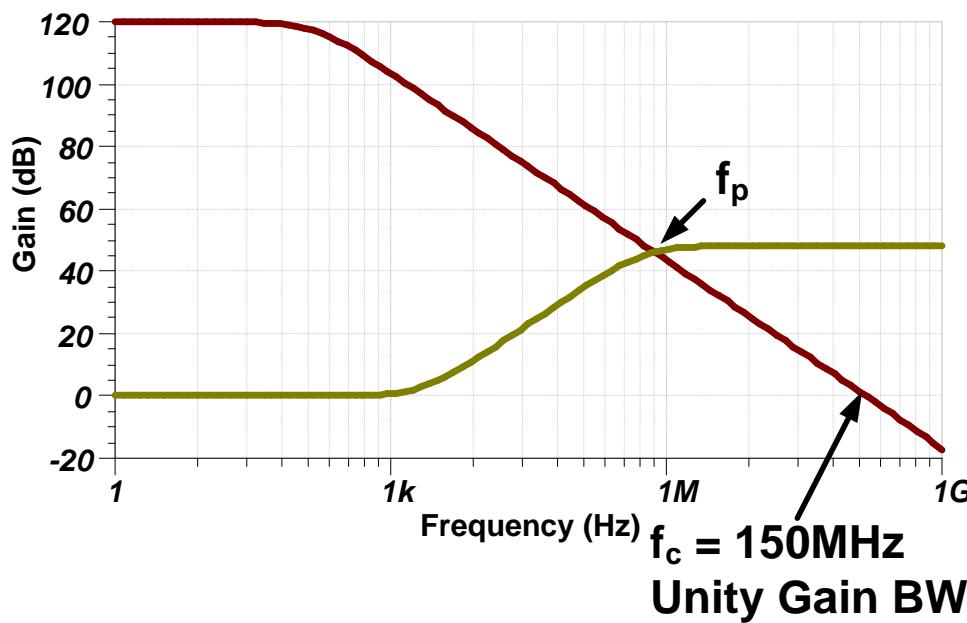More exact formula for feedback capacitance



Op Amp Calculations

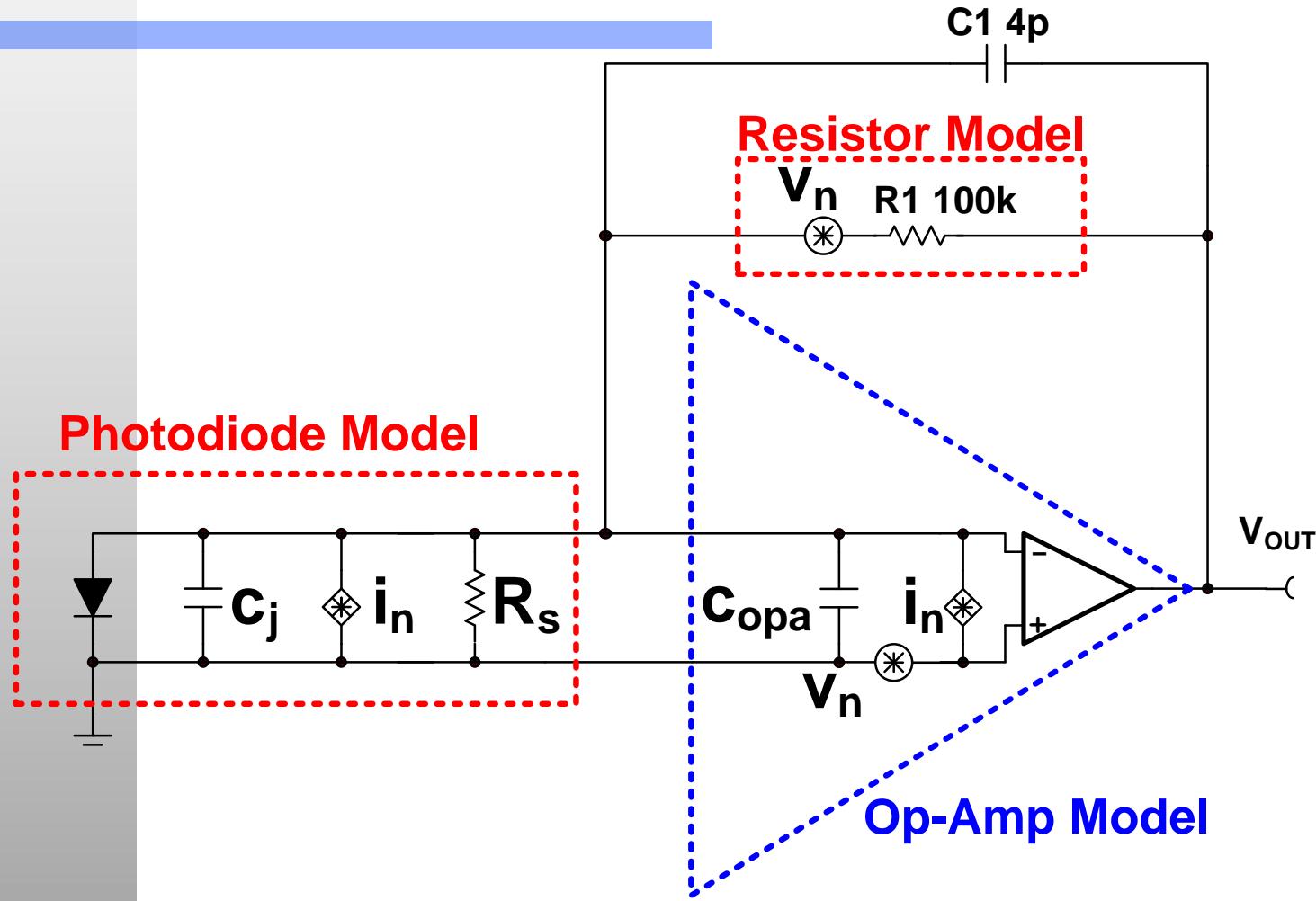Noise Model for Simple Transimpedance Amp




Example Photodiode: PDB-C158

ABSOLUTE MAXIMUM RATING (TA)= 23°C UNLESS OTHERWISE NOTED

SYMBOL	PARAMETER	MIN	MAX	UNITS
V_{BR}	Reverse Voltage		50	V
T_{STG}	Storage Temperature	-40	+100	°C
T_o	Operating Temperature	-40	+80	°C
T_s	Soldering Temperature*		+260	°C

* 1/16 inch from case for 3 seconds max.

SPECTRAL RESPONSE

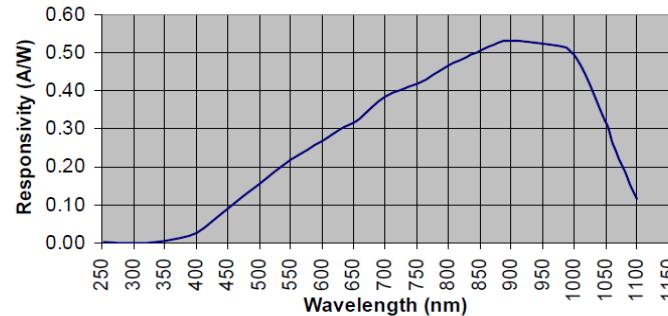

ELECTRO-OPTICAL CHARACTERISTICS RATING (TA)= 23°C UNLESS OTHERWISE NOTED

SYMBOL	CHARACTERISTIC	TEST CONDITIONS	MIN	TYP	MAX	UNITS
I_{SC}	Short Circuit Current	$H = 100 \text{ fc}, 2850 \text{ K}$	100	145		μA
I_D	Dark Current	$V_R = 10 \text{ V}$		2	30	nA
R_{SH}	Shunt Resistance	$V_R = 10 \text{ mV}$	100	150		MΩ
C_J	Junction Capacitance	$V_R = 10 \text{ V}, f = 1 \text{ MHz}$		10	25	pF
Range	Spectral Application Range	Spot Scan	400	1100		nm
V_{BR}	Breakdown Voltage	$I = 10 \mu\text{A}$	30	75		V
NEP	Noise Equivalent Power	$V_R = 10 \text{ V} @ \lambda = \text{Peak}$		4.4×10^{-14}		$\text{W}/\sqrt{\text{Hz}}$
t_r	Response Time	$RL = 1\text{K}\Omega, V_R = 10 \text{ V}$		50		nS

**Response time of 10% to 90% is specified at 660nm wavelength light.

C_j is not specified at V_r=0V.

C_j=70pF for V_r=0V

Calculate Diode Current Noise

Thermal (Johnson Noise)

$$\sqrt{\frac{4k_b \cdot T_n}{R_{sh}}} = 10.472 \times 10^{-15} \frac{A}{\sqrt{Hz}}$$

Shot noise (dark)

$$\sqrt{2q \cdot I_D} = 25.314 \times 10^{-15} \cdot \frac{A}{\sqrt{Hz}}$$

Shot noise (w. Light)

$$i_{sL} := \sqrt{2q \cdot I_L} = 0$$

Total Diode Current Noise

$$\sqrt{i_j^2 + i_{sD}^2 + i_{sL}^2} = 27.395 \times 10^{-15} \cdot \frac{A}{\sqrt{Hz}}$$

$$k_b := 1.38 \cdot 10^{-23} \frac{J}{K}$$

$$q := 1.602 \cdot 10^{-19} C$$


$$T_n := 298 K$$

$$f_p := 397.887 \times 10^3 \text{ Hz}$$


$$R_{sh} := 150 \cdot 10^6 \Omega$$

$$I_D := 2 \cdot 10^{-9} A$$


$$I_L := 0 A$$

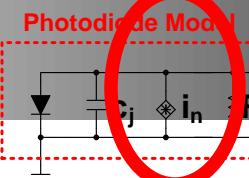

Photodiode Model

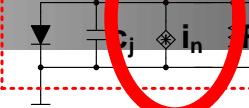

Resistor Model

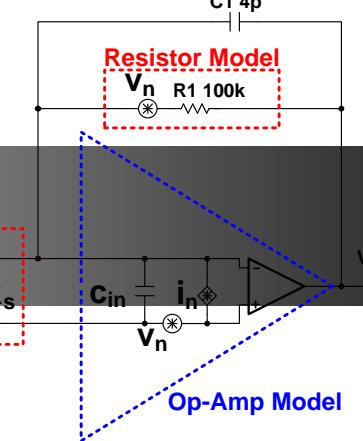

Op-Amp Model

Boltzmann constant

One electron Charge

Temperature in Kelvin (25C)


Transconductance bandwidth

Shunt Resistance in photodiode

Dark Current in photodiode

Photo current in photodiode
(our measurements are dark)

OPA827 Noise Calculation (key numbers)

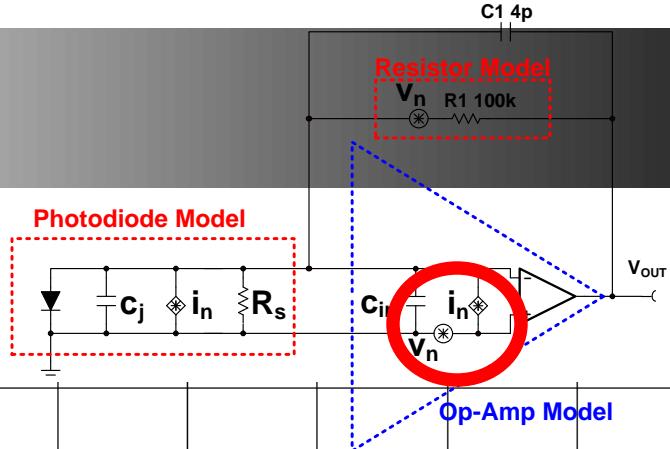

NOISE							
Input Voltage Noise:							
$f = 0.1\text{Hz to } 10\text{Hz}$	e_n	$V_S = \pm 18V, V_{CM} = 0V$		250		250	nV_{PP}
Input Voltage Noise Density:							
$f = 1\text{kHz}$	e_n	$V_S = \pm 18V, V_{CM} = 0V$		4		4	$nV/\sqrt{\text{Hz}}$
$f = 10\text{kHz}$	e_n	$V_S = \pm 18V, V_{CM} = 0V$		3.9		3.8	$nV/\sqrt{\text{Hz}}$
Input Current Noise Density:							
$f = 1\text{kHz}$	i_n	$V_S = \pm 18V, V_{CM} = 0V$		2.2		2.2	$fA/\sqrt{\text{Hz}}$
INPUT IMPEDANCE							
Differential				$10^{13} \parallel 9$		$10^{13} \parallel 9$	$\Omega \parallel pF$
Common-Mode				$10^{13} \parallel 9$		$10^{13} \parallel 9$	$\Omega \parallel pF$
OPEN-LOOP GAIN							
Open-Loop Voltage Gain	A_{OL}	$(V-) + 3V \leq V_O \leq (V+) - 3V, R_L = 1k\Omega$	120	126	120	126	dB
Over Temperature		$(V-) + 3V \leq V_O \leq (V+) - 3V, R_L = 1k\Omega$	114		114		dB
FREQUENCY RESPONSE							
Gain-Bandwidth Product	GBW	$G = +1$		22		22	MHz

OPA827 Noise Hand Calculation

$$C_j := 70\text{pF}$$

Photodiode Junction Capacitance
(from photodiode manufacturer)

$$C_{opa} := 18\text{pF}$$

Opamp input capacitance
(OPA827 Data Sheet)

$$C_i := C_j + C_{opa}$$

Total input capacitance

$$f_c := 22\text{MHz}$$

Unity Gain Bandwidth
(OPA827 Data Sheet)

$$R_f := 100\text{k}\Omega$$

Feedback resistance

$$C_f := 4\text{pF}$$

Feedback capacitor

$$e_{nif} := 3.8 \frac{\text{nV}}{\sqrt{\text{Hz}}}$$


Broadband Noise Spectral Density
(OPA827 Data Sheet)

$$f_L := .1\text{Hz}$$

Lower bound on frequency (1/f region)
(arbitrary lower bound of frequency)

$$e_{at_f} := 60 \frac{\text{nV}}{\sqrt{\text{Hz}}}$$

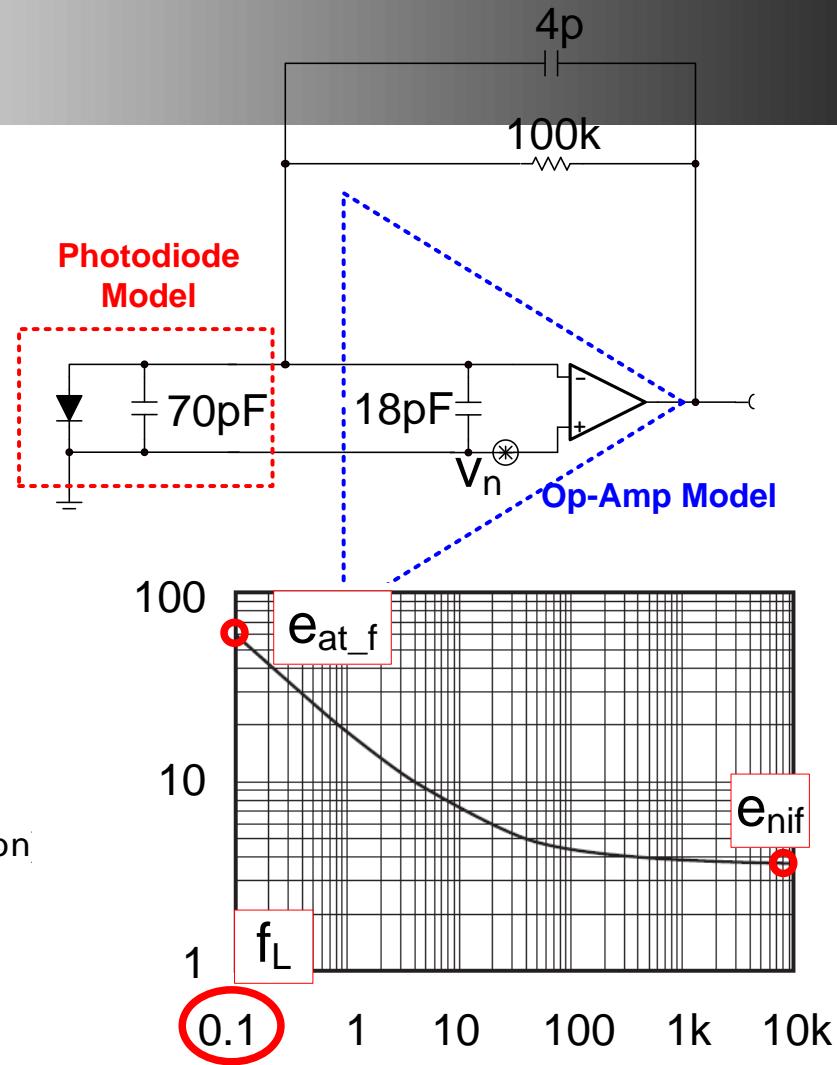Flicker noise measured at f_L
(OPA827 Data Sheet Noise Curve)




Poles and Zeros in Noise Gain Curve

$$f_z := \frac{1}{2\pi R_f \cdot (C_i + C_f)} = 17.299 \times 10^3 \text{ Hz}$$

$$f_p := \frac{1}{2\pi R_f \cdot C_f} = 397.887 \times 10^3 \text{ Hz}$$
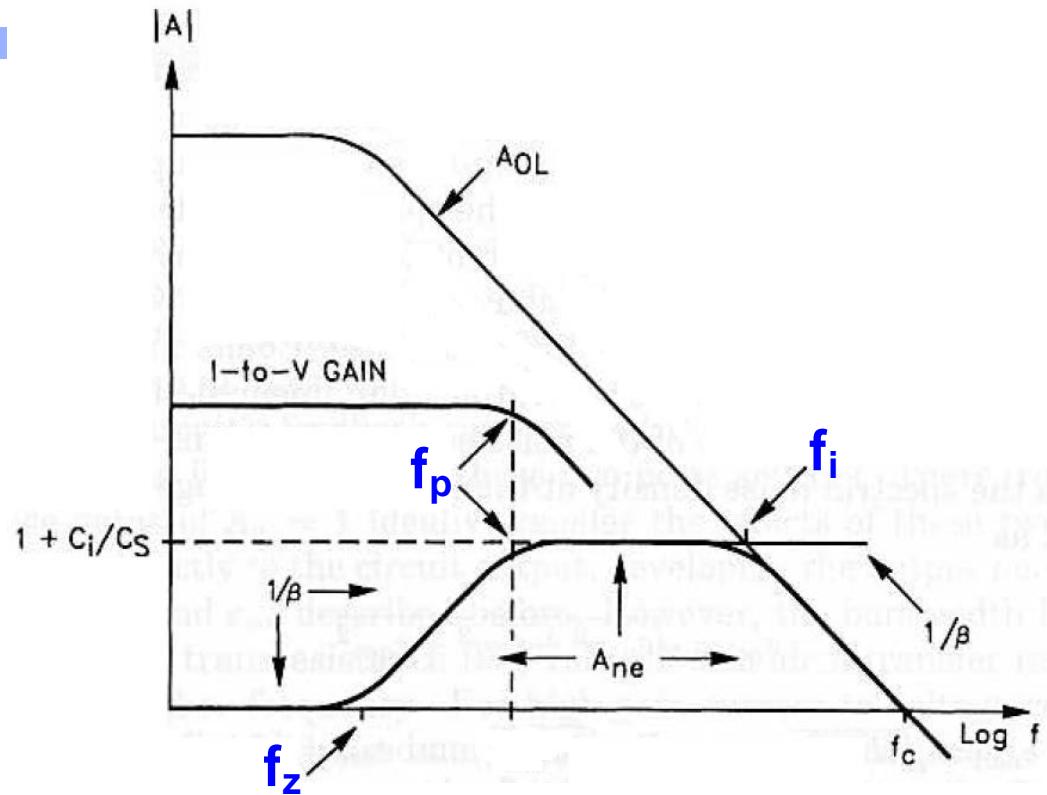
$$f_i := \frac{C_f}{C_i + C_f} \cdot f_c = 956.522 \times 10^3 \text{ Hz}$$



Output Noise from OPA Noise Voltage

$$E_{noe1} := \sqrt{e_{nif}^2 \cdot f_f \cdot \ln\left(\frac{f_f}{f_L}\right)} = 44.573 \times 10^{-9} \text{ V}$$


$$E_{noe2} := \sqrt{e_{nif}^2 \cdot (f_z - f_f)} = 499.444 \times 10^{-9} \text{ V}$$

$$E_{noe3} := \sqrt{\left(\frac{e_{nif}}{f_z}\right)^2 \cdot \frac{f_p^3 - f_z^3}{3}} = 31.828 \times 10^{-6} \text{ V}$$

$$E_{noe4} := \sqrt{\left(e_{nif} \cdot \frac{C_i + C_f}{C_f}\right)^2 \left(f_i - f_p\right)} = 65.324 \times 10^{-6} \text{ V}$$

$$E_{noe5} := \sqrt{\frac{(e_{nif} \cdot f_c)^2}{f_i}} = 85.479 \times 10^{-6} \text{ V}$$
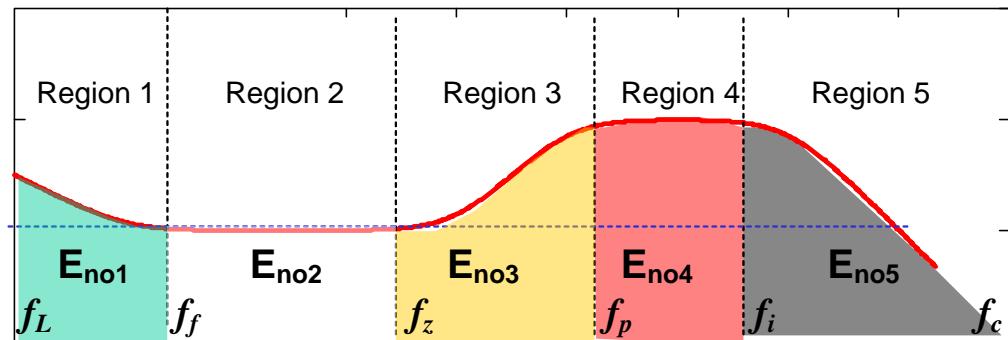
$$E_{noe} := \sqrt{E_{noe1}^2 + E_{noe2}^2 + E_{noe3}^2 + E_{noe4}^2 + E_{noe5}^2} = 112.193 \times 10^{-6} \text{ V}$$



Thermal (Resistor) Noise at Output

$$R_f := 100 \cdot 10^3 \Omega$$

Feedback Resistance

$$k_b := 1.38 \cdot 10^{-23} \frac{\text{J}}{\text{K}}$$

Boltzmann constant

$$T_n := 298 \text{ K}$$

Temperature in Kelvin (25C)

$$f_p := 397.887 \times 10^3 \text{ Hz}$$

Transconductance bandwidth

$$K_n := 1.57$$


Noise Current from OPA827 data sheet

$$BW_n := K_n \cdot f_p$$

Noise bandwidth (brick wall filter)

$$e_{n_r} := \sqrt{4k_b \cdot T_n \cdot R_f \cdot BW_n} = 32.056 \times 10^{-6} \text{ V}$$

Thermal noise at output

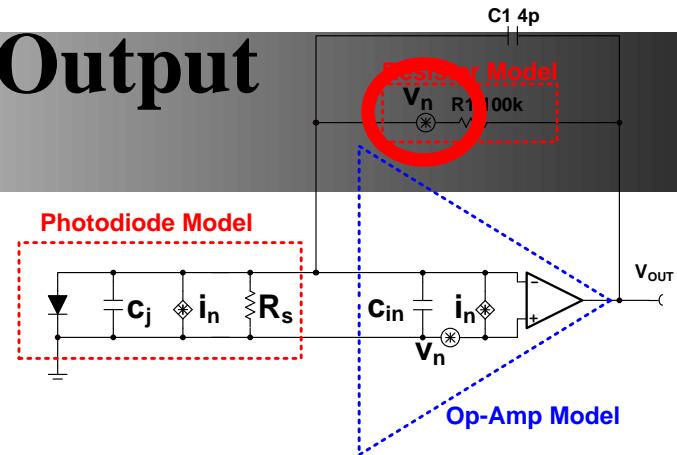

Current Noise to Voltage Noise at Output

$$R_f := 100 \cdot 10^3 \Omega$$

Feedback Resistance

$$f_p := 397.887 \times 10^3 \text{ Hz}$$

Transconductance bandwidth

$$i_{n_opa} := 2.2 \times 10^{-15} \frac{\text{A}}{\sqrt{\text{Hz}}}$$

Noise Current from OPA827 data sheet

$$i_{n_diode} := 27.395 \times 10^{-15} \frac{\text{A}}{\sqrt{\text{Hz}}}$$

$$i_{n_total} := \sqrt{i_{n_opa}^2 + i_{n_diode}^2}$$

$$K_n := 1.57$$

$$BW_n := K_n \cdot f_p = 6.247 \times 10^5 \text{ Hz}$$

Noise Current from diode (calculated)


Total Noise Current

Noise bandwidth factor
1st order filter

Noise bandwidth (brick wall filter)

$$E_{noise} := i_{n_total} \cdot R_f \cdot \sqrt{BW_n} = 2.172 \times 10^{-6} \text{ V}$$

Current noise at output

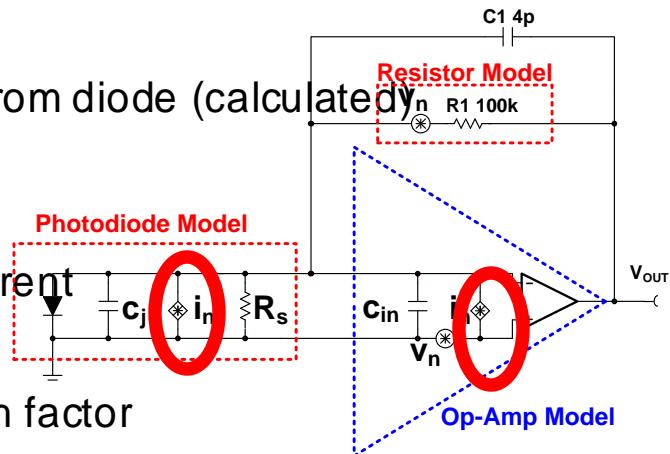

The Final Total Noise

$$E_{noe} := 112.193 \times 10^{-6} \text{ V} \quad \text{Op-Amp Voltage Noise}$$





$$E_{noR} := 32.056 \times 10^{-6} \text{ V} \quad \text{Resistor Noise}$$

$$E_{noI} := 2.172 \times 10^{-6} \text{ V} \quad \text{Op-Amp Current Noise}$$

$$E_{no} := \sqrt{E_{noR}^2 + E_{noI}^2 + E_{noe}^2} = 116.703 \times 10^{-6} \text{ V}$$


Total Output Noise for
OPA827 Transimpedance Amp

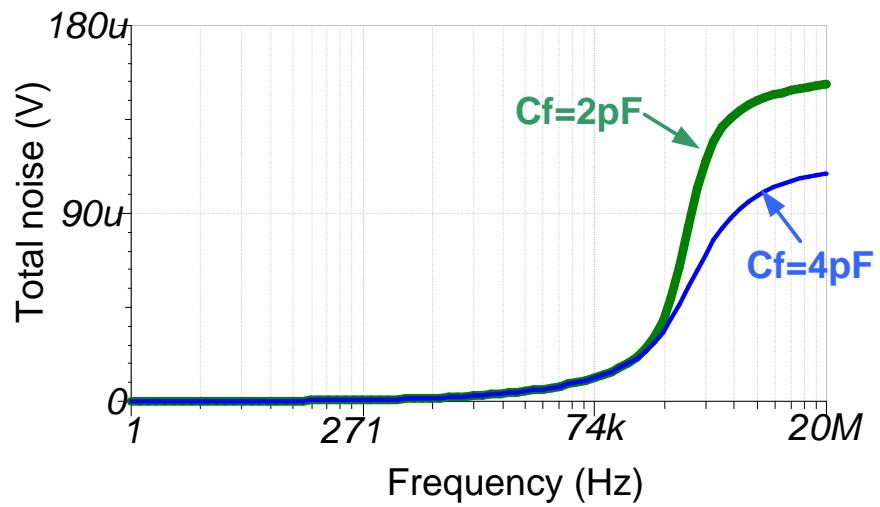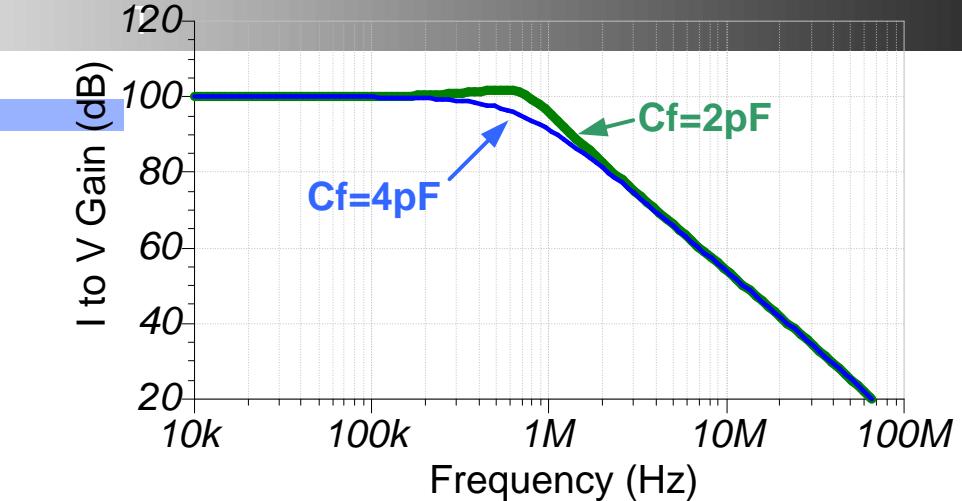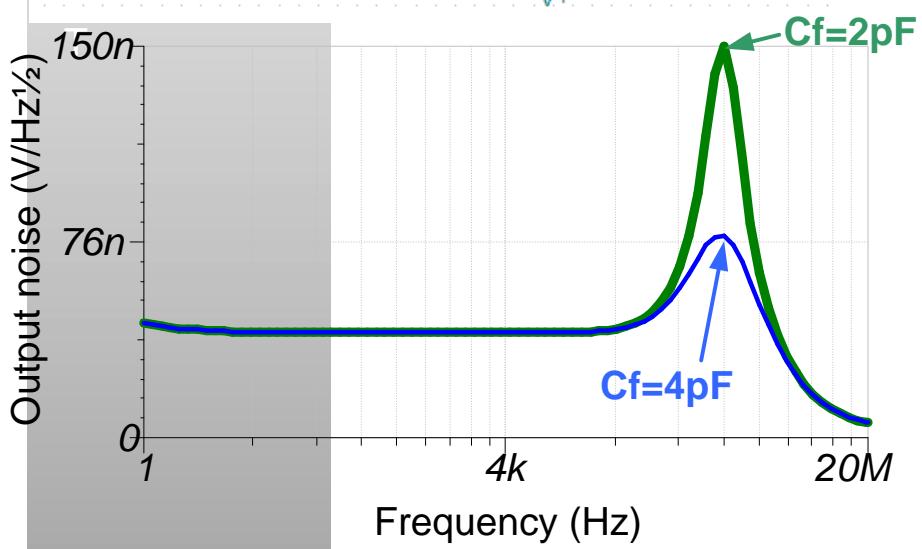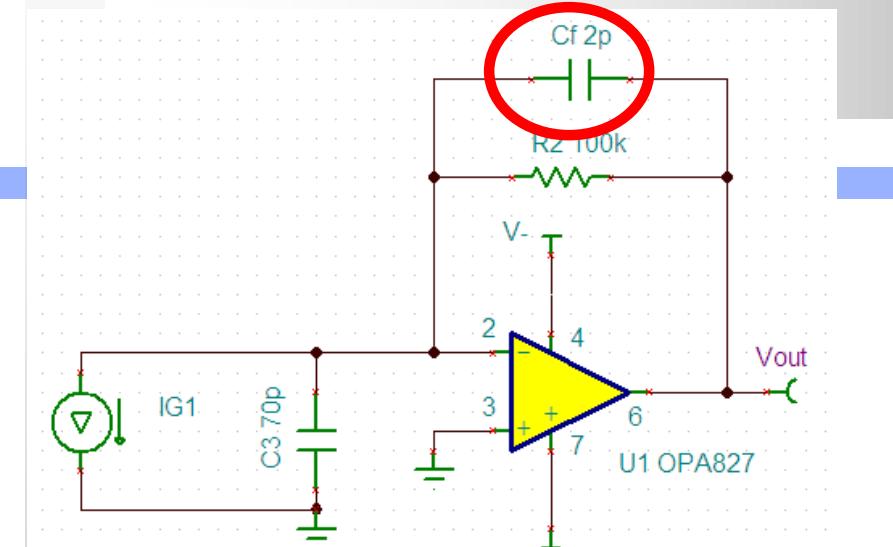Reducing Noise (Higher Cf = Lower BW Noise)



OPA827 Spice Analysis

OPA827 – test the model

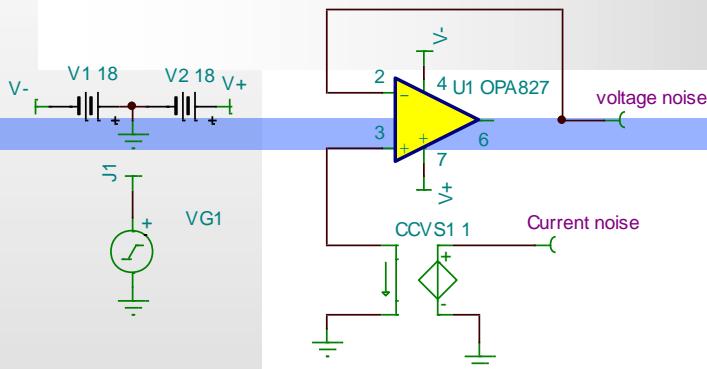

- ◆ Low Noise : $4\text{nV}/\sqrt{\text{Hz}}$ at 1kHz
- ◆ Low Offset Voltage: $150\mu\text{V}$ max
- ◆ JFET Input: $I_B = 15\text{pA}$ typ
- ◆ Wide Bandwidth: 22MHz

The voltage noise performance
is the same as datasheet.



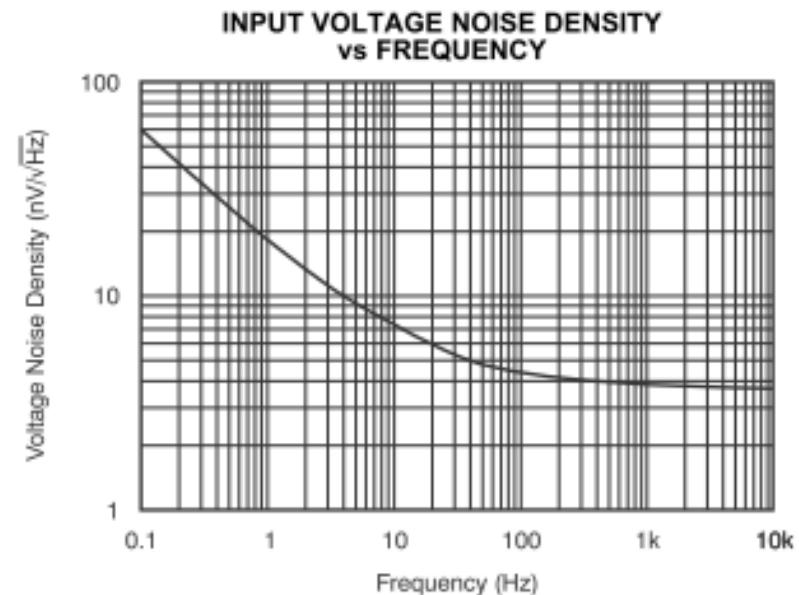
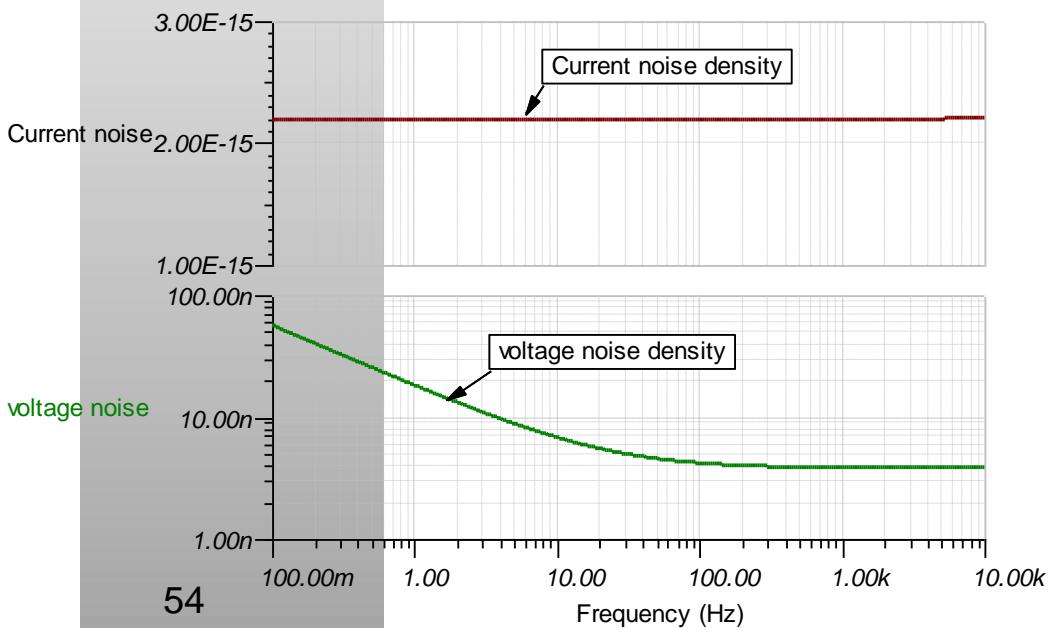


Figure 1.

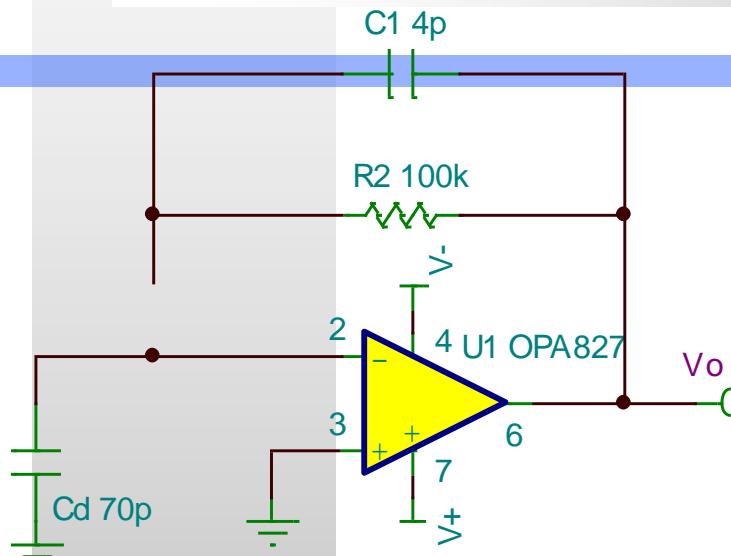Simulated Spectral Density and Total Noise




Calculated (rms)	Simulated (rms)
116.7 μ V	109.1 μ V

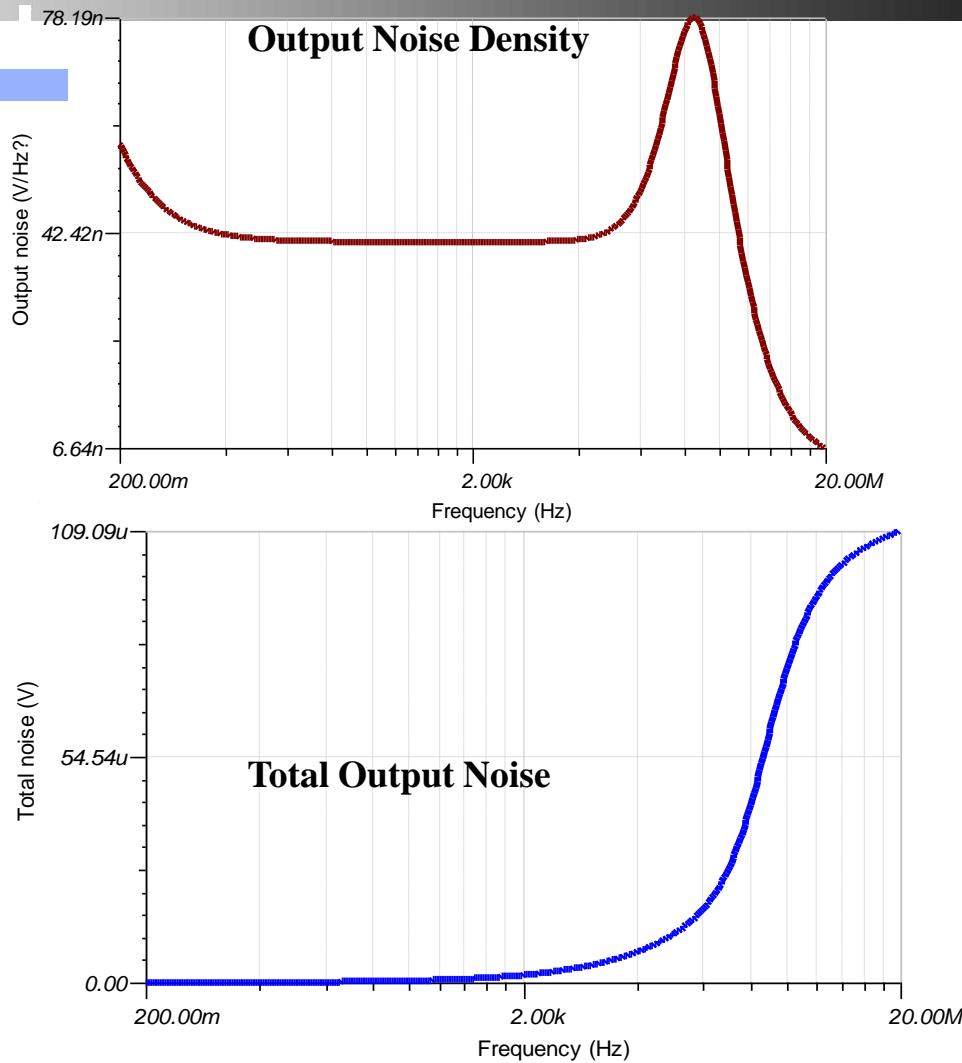

Op Amp Measurement Example

Validating Test Equipment Capability

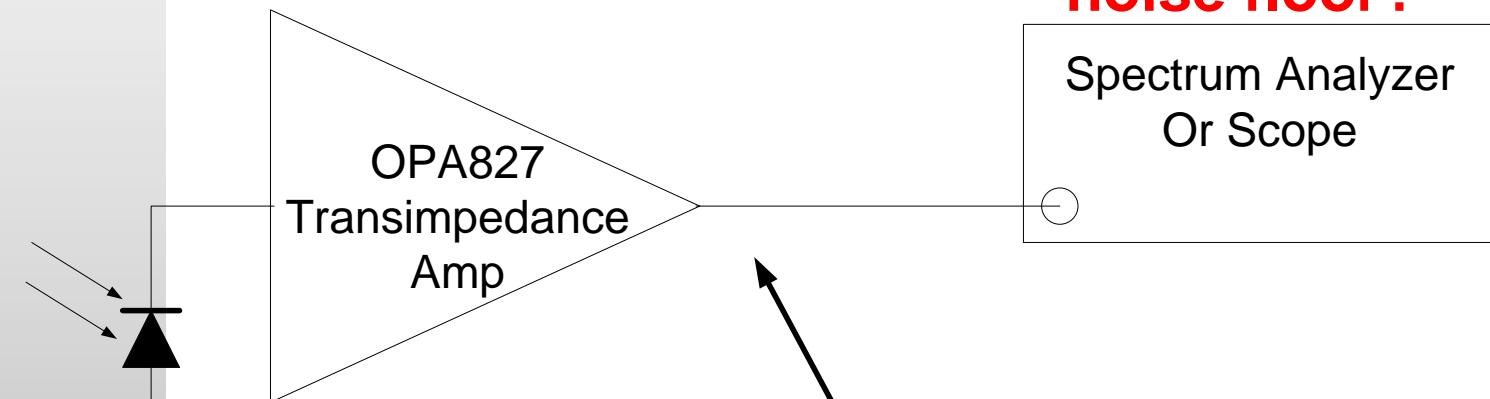


What is the
noise floor?

Spectrum Analyzer
Or Scope

Photodiode
(No light)

Noise Spectral Density = 3.8nV/rtHz
Total Noise = $109.1\mu\text{Vrms}$
 $= 654.6\mu\text{Vp-p}$

Tektronix DPO 4034 Oscilloscope

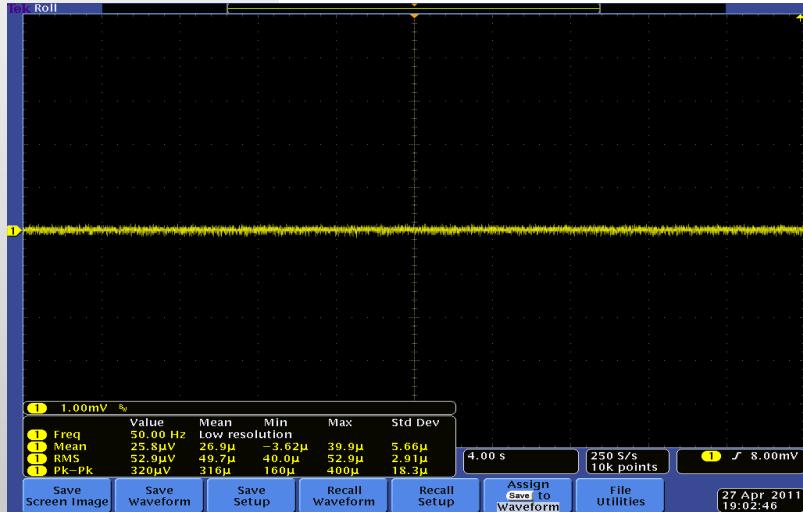


STDEV: 48uV (same as RMS)
P-P: 6.6*STDEV=319uV
40s P-P: 320uV


- 1) Set DC couple, 20MHz bandwidth limit
- 2) Short input channel to measure noise floor

Agilent 4395A Spectrum Analyzer

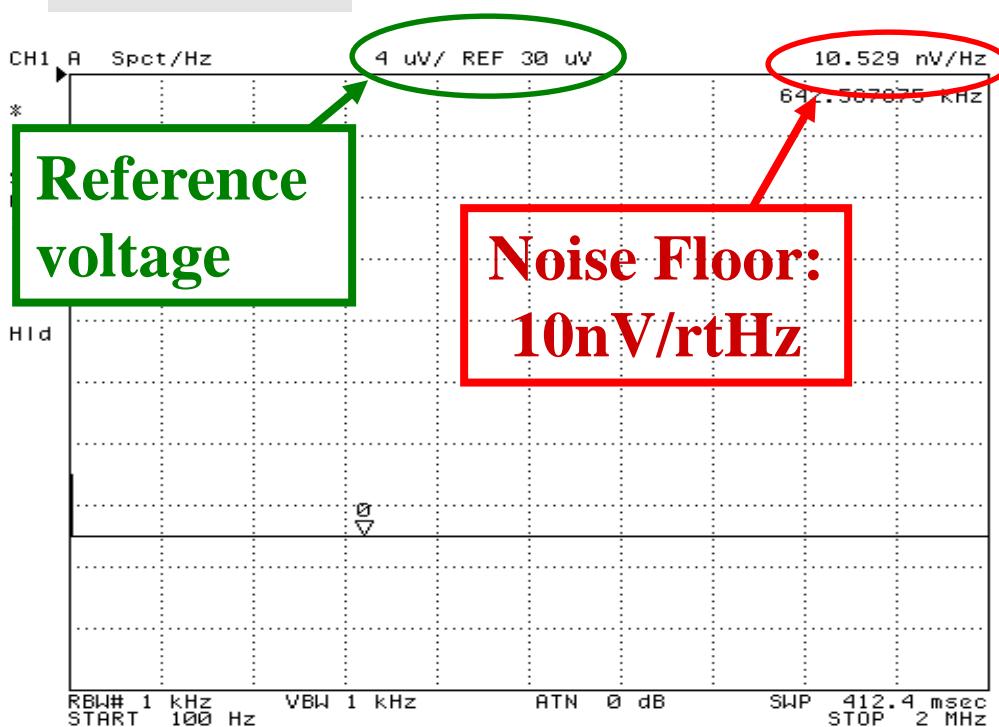1. Frequency Range: 10Hz~500MHz
2. Noise floor: 10nV/rtHz
3. Input Impedance: 50Ω




The Noise Floors are Not Good Enough

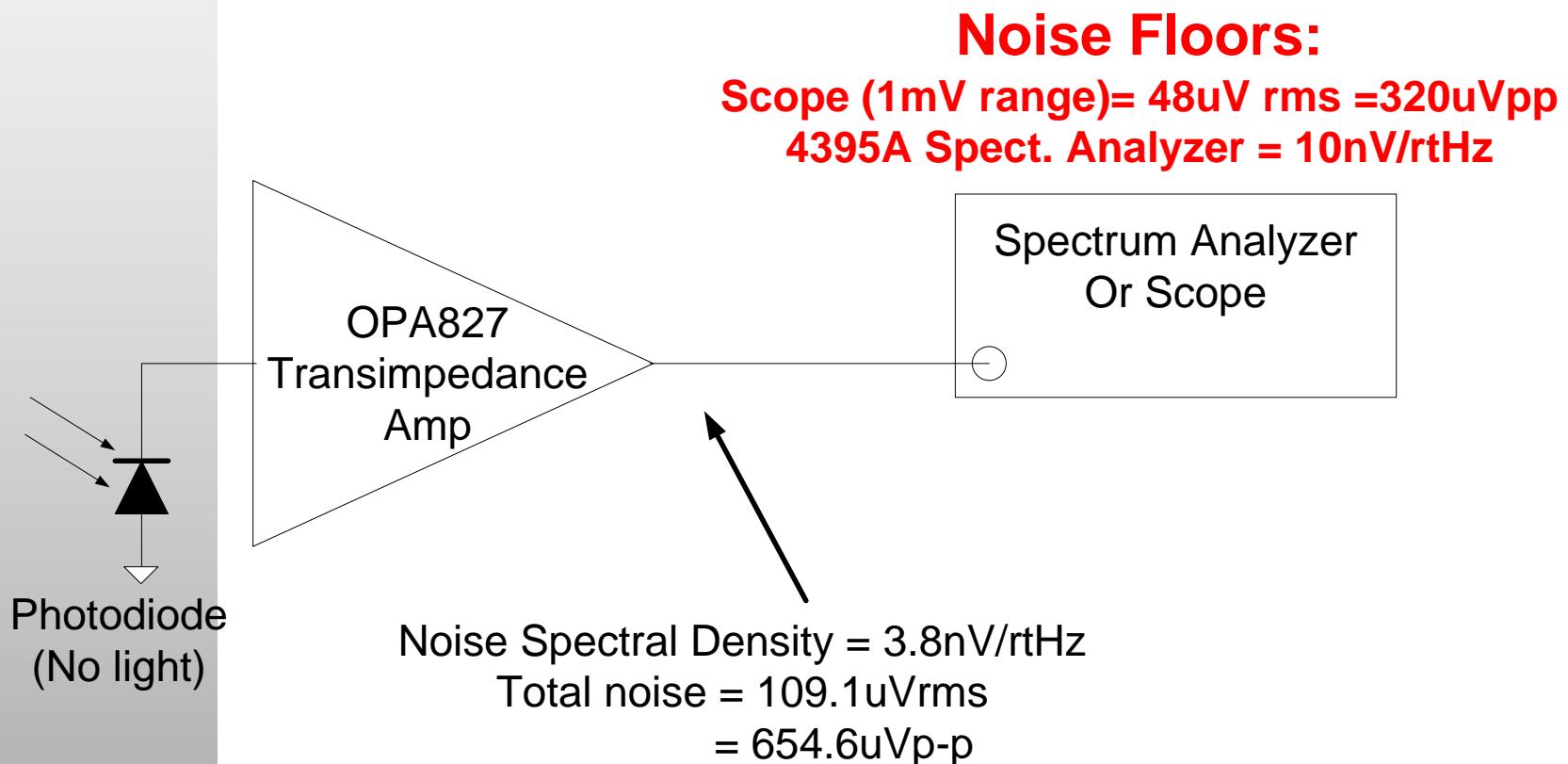

Solution: Use A Post Amp


What amp do we Choose?

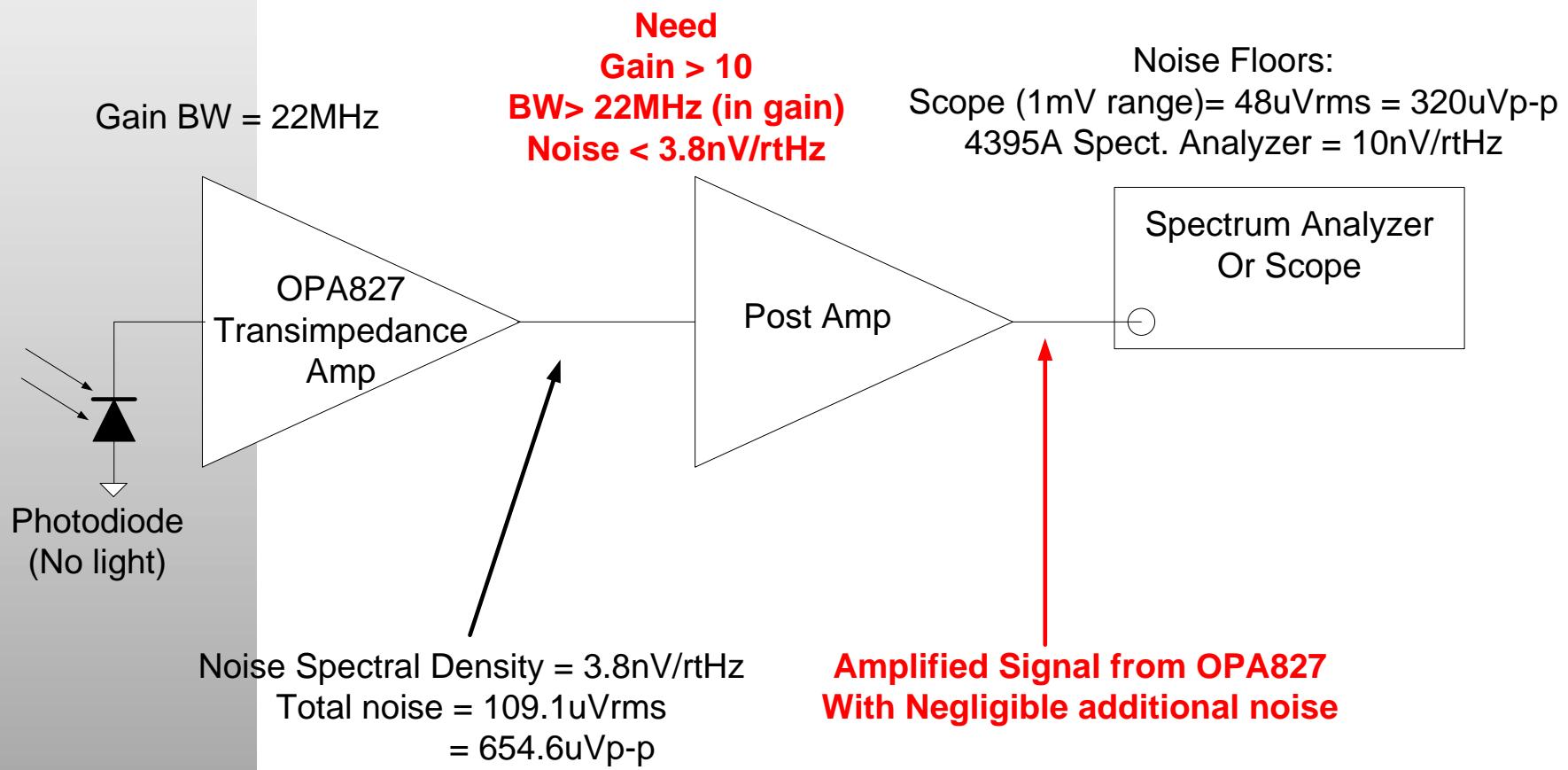



OPA847 as post amplifier

Wideband, Ultra-Low Noise, Voltage Feedback, Operational Amplifier

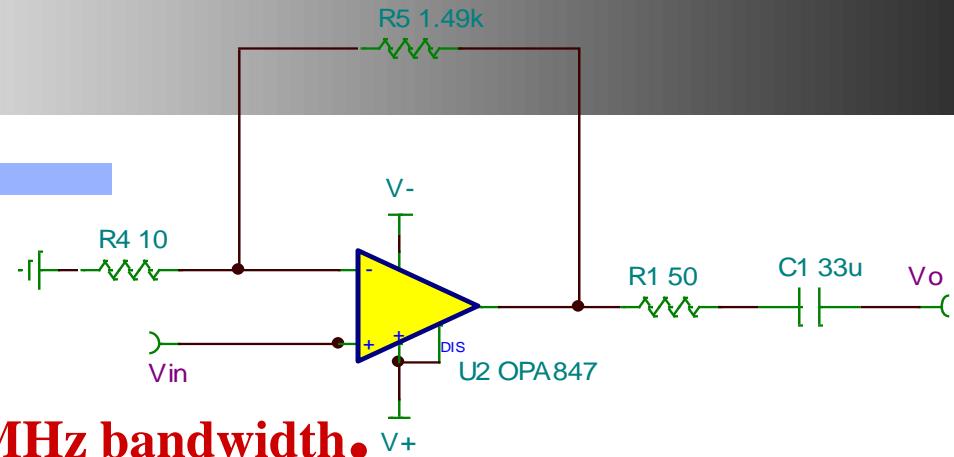- At the gain of 150, the bandwidth is 26MHz
- 0.85nV/ $\sqrt{\text{Hz}}$ Input Voltage Noise
- 2.5pA/ $\sqrt{\text{Hz}}$ Input Current Noise
- $\pm 100\mu\text{V}$ Input Offset Voltage (Typical))





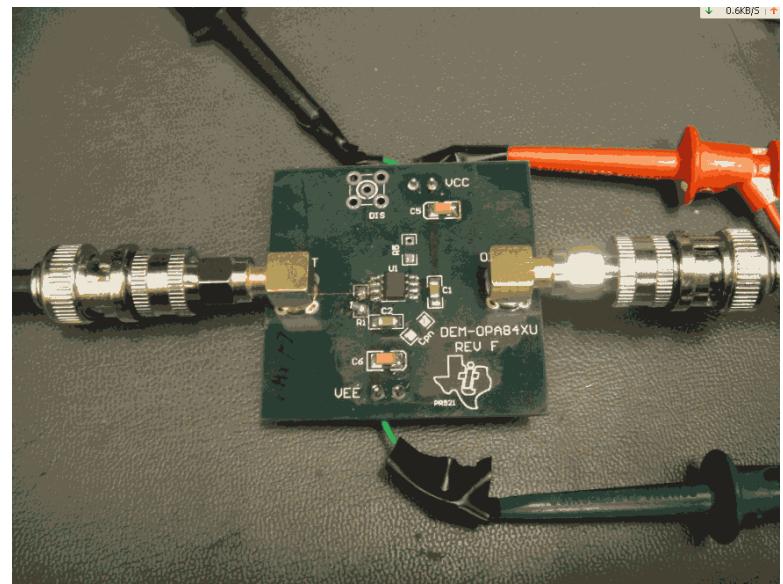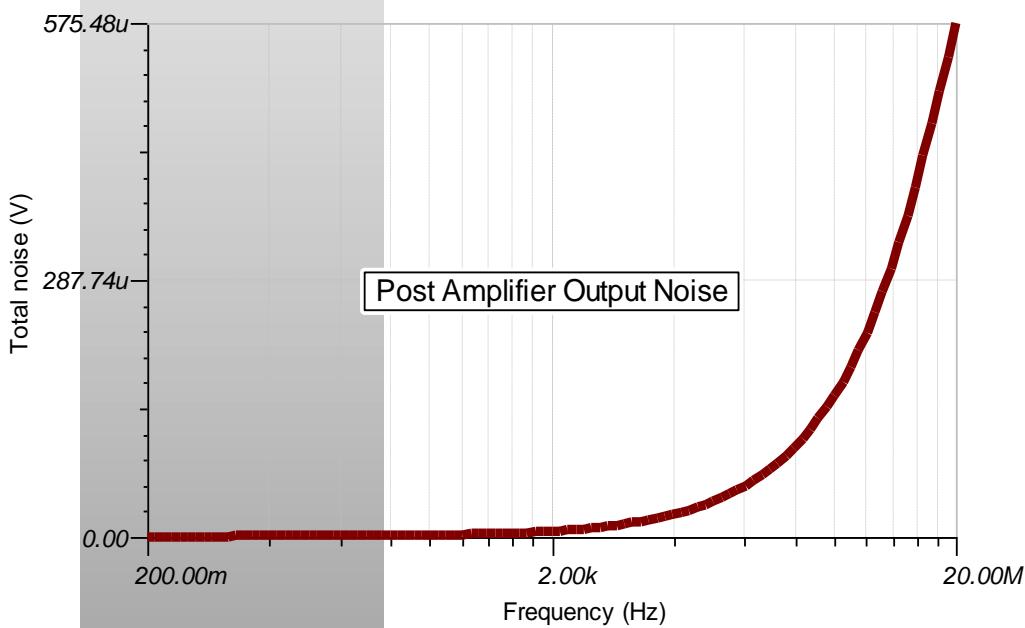575uVrms post amplifier noise in 20MHz bandwidth.



Post Amplifier Relatively small error!

Gain=150

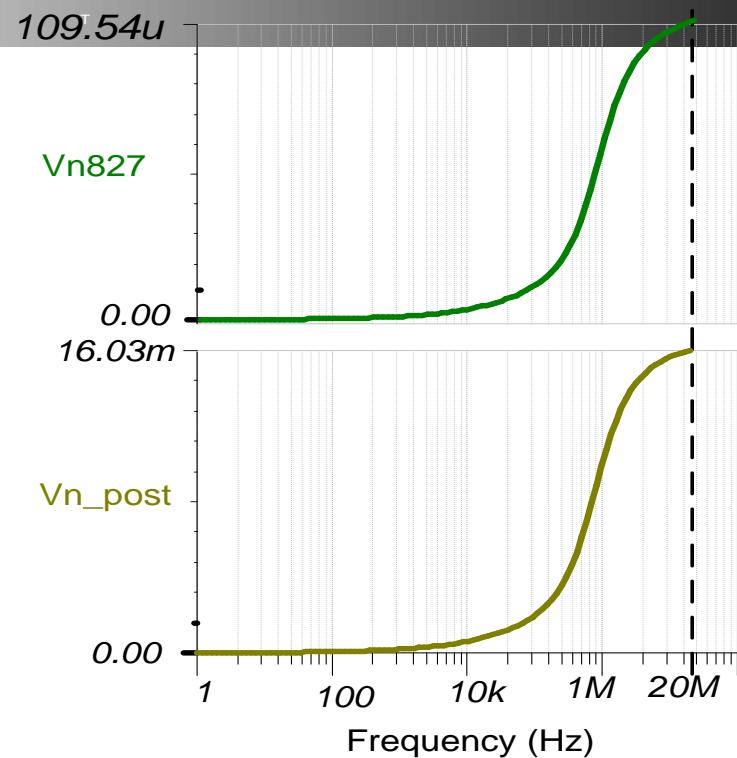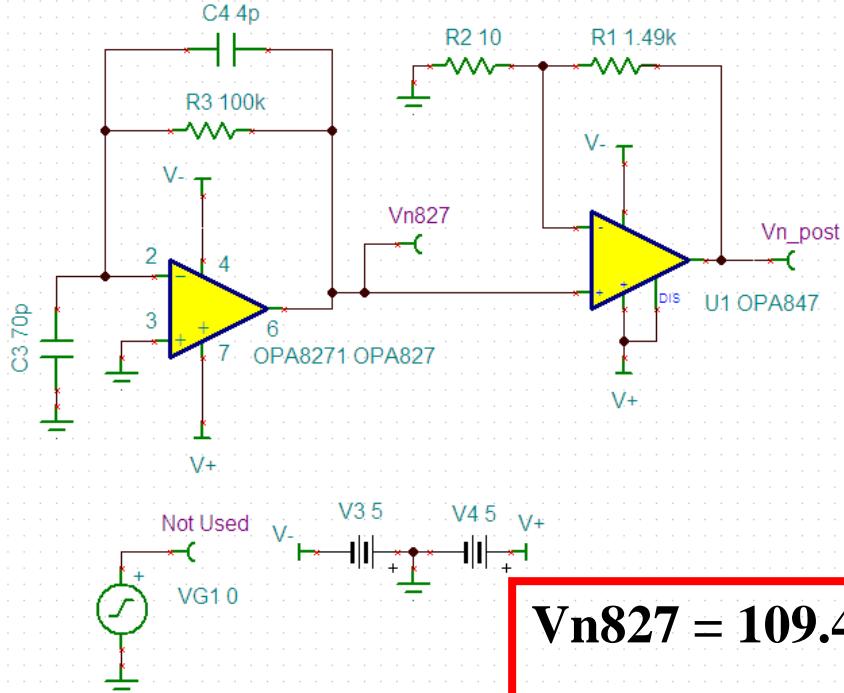


$$Vn827 = 109.4\mu V \text{ rms}$$


$$Vnpost = 16.03mV \text{ rms}$$

$$Vnpost/Gain = 16.03mV/150 = 106.8\mu V \\ \text{rms}$$

Test the Noise Floor

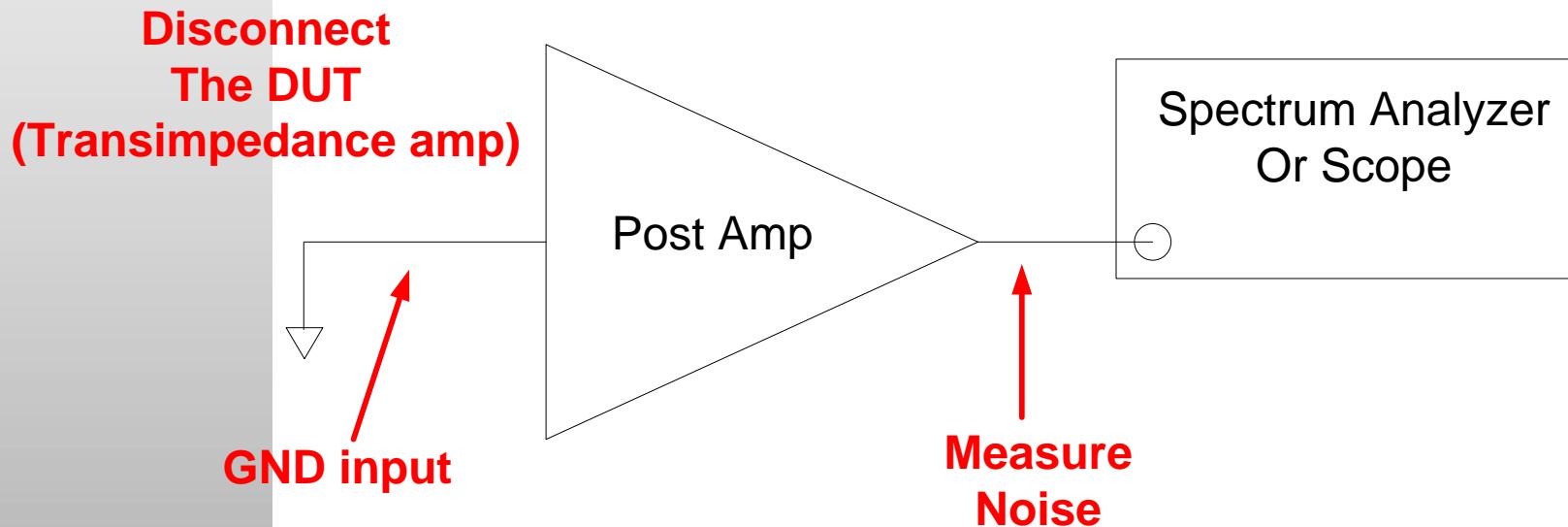

Test The Noise Floor – Post Amp Noise

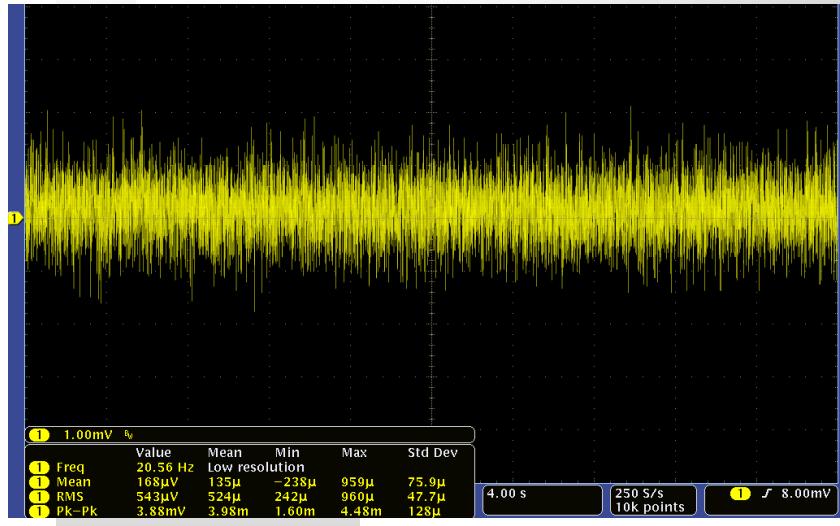


Simulated (rms)	Measured (rms)
575 μV	518 μV


STDEV: 518 μV

P-P: 6.6 * STDEV = 3.4 mV


40s P-P: 3.88 mV

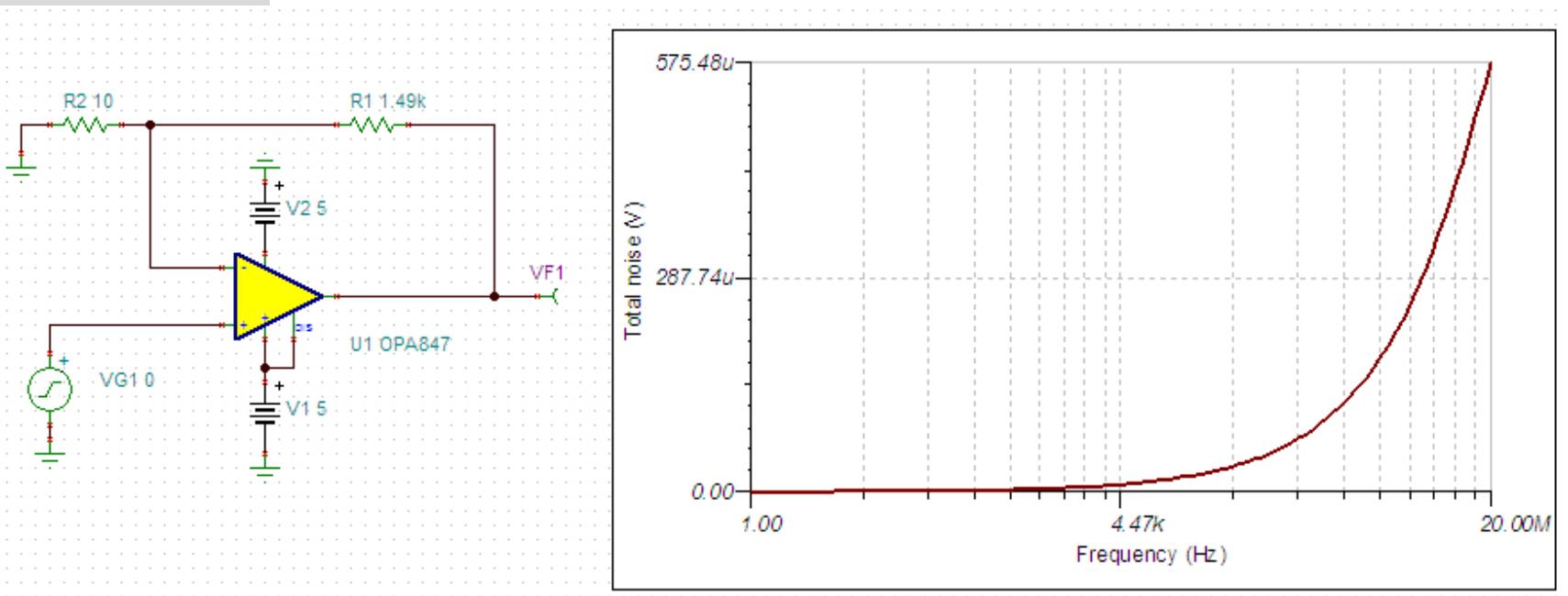



Hardware Connections

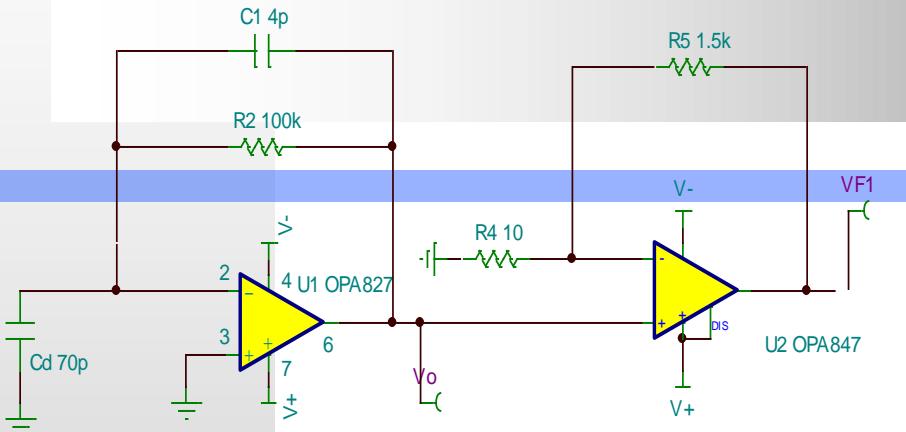

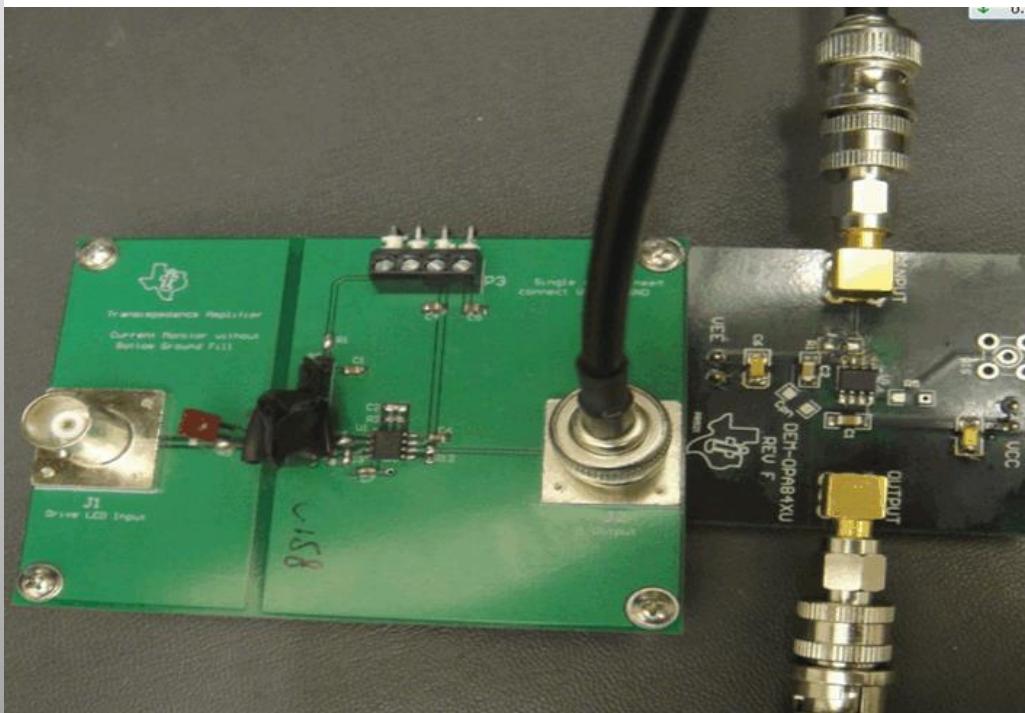
1. PDB-C158-ND photodiode
2. 70pF junction capacitance at $V_r=0$ V
3. 100dB I-V gain
4. 4pF compensation capacitor
5. ± 5 V power supply.





Divide by Gain for OPA827 Output Noise

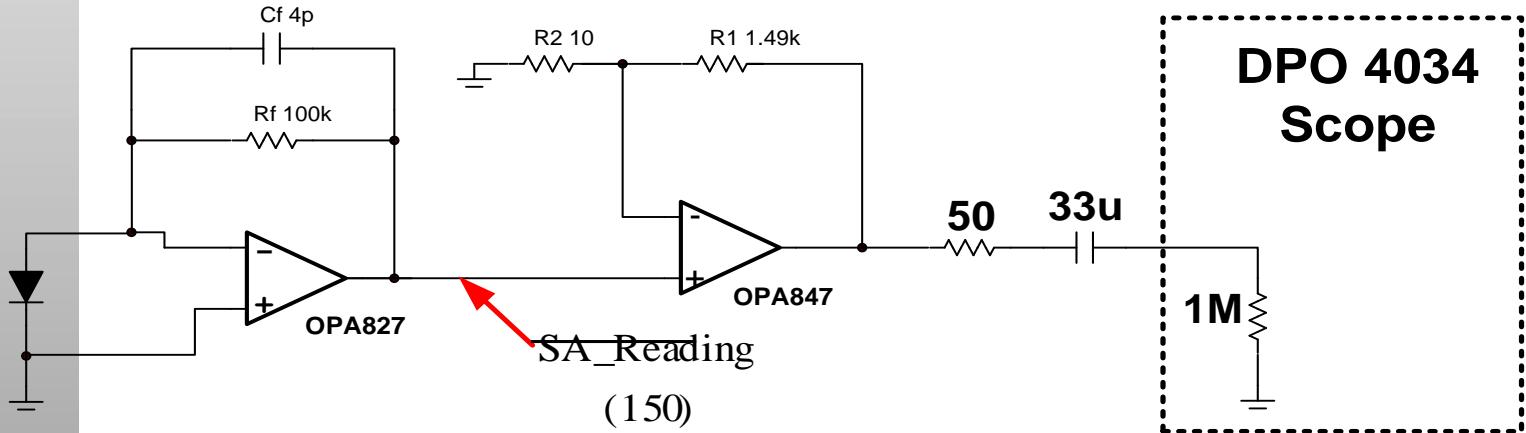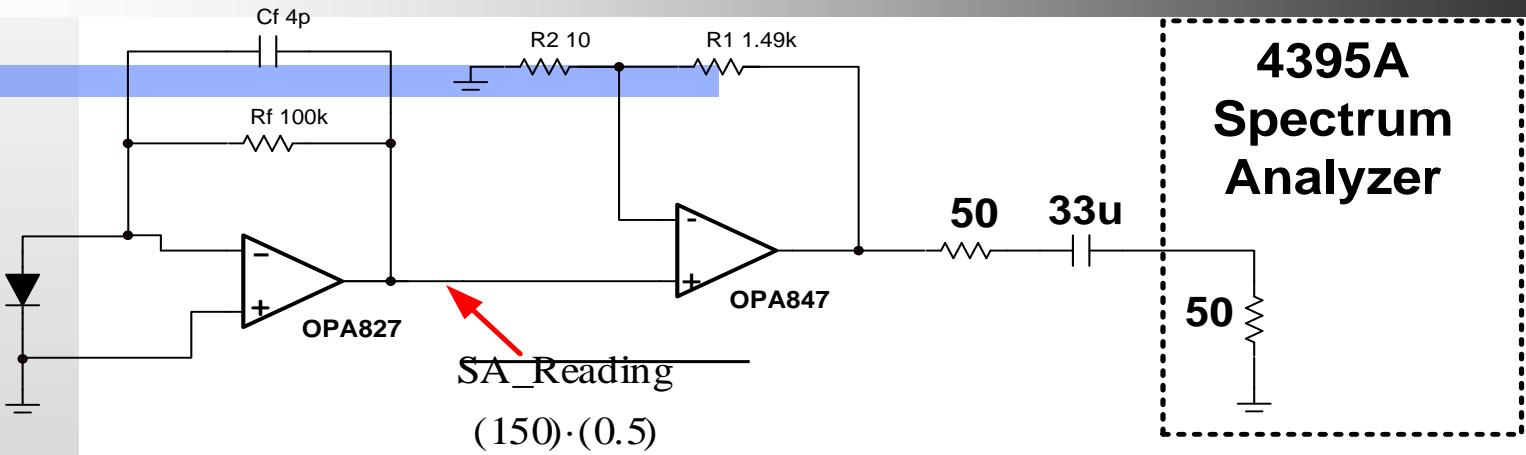


Measured Spectral Density 4395A Spectrum

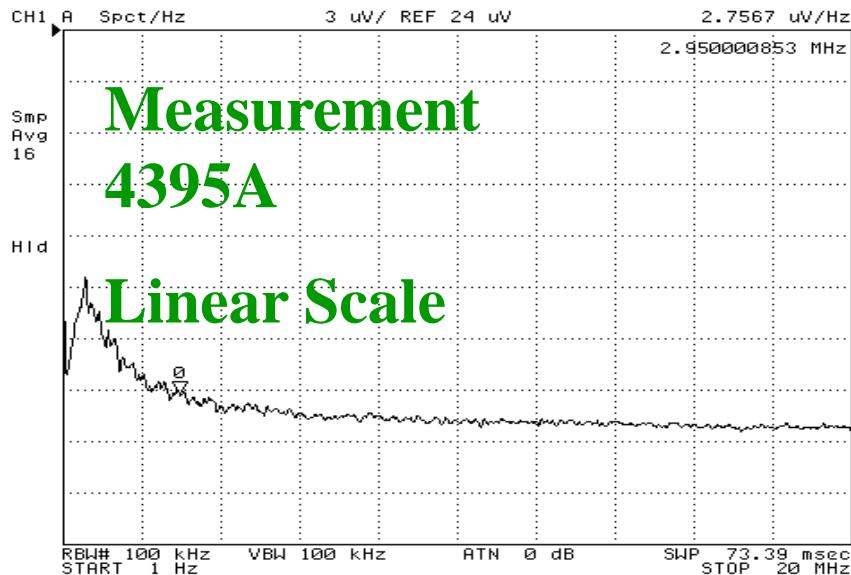

1. Agilent 4395A Spectrum Analyzer test **1Hz~20MHz** span, **3uV/div**, **REF=24uV**.
2. The tested noise density curve shape is the same as simulation.

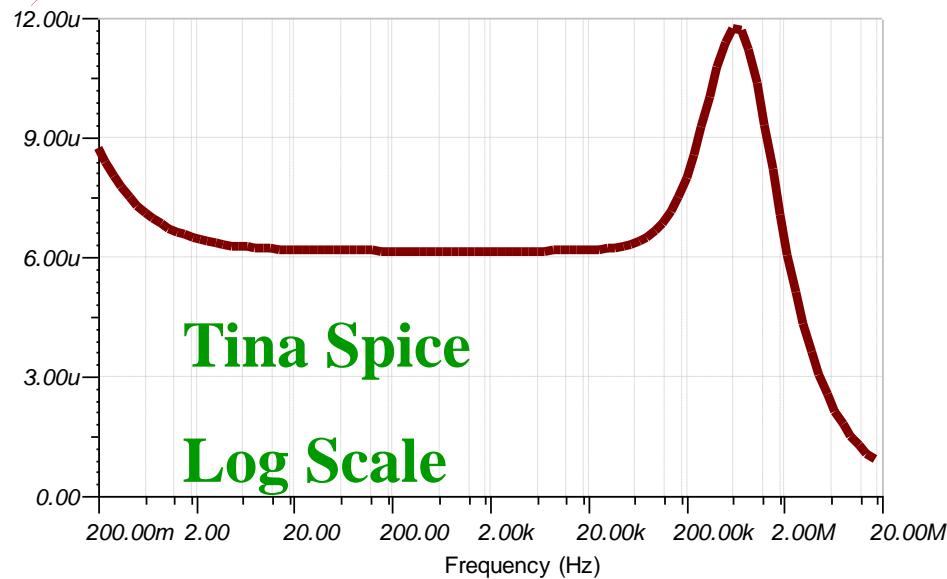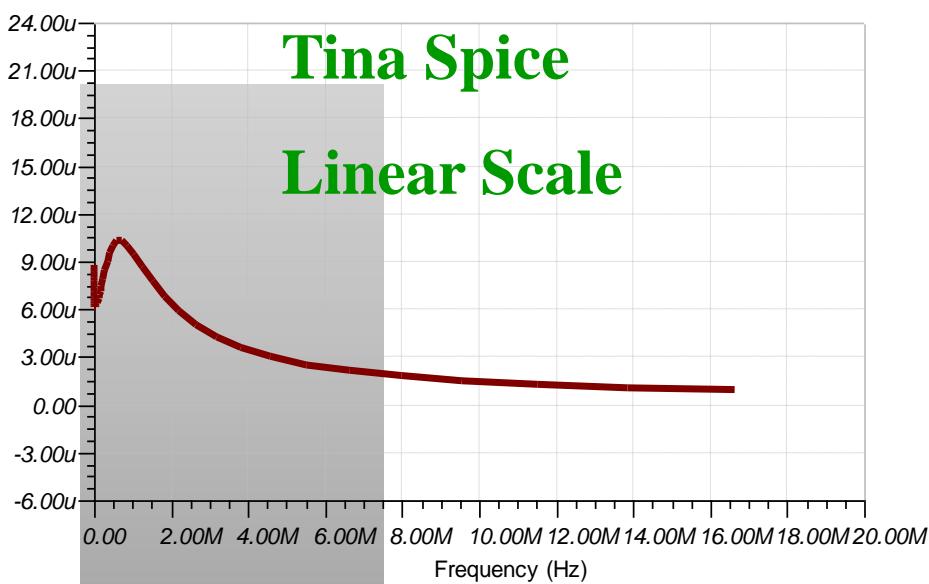

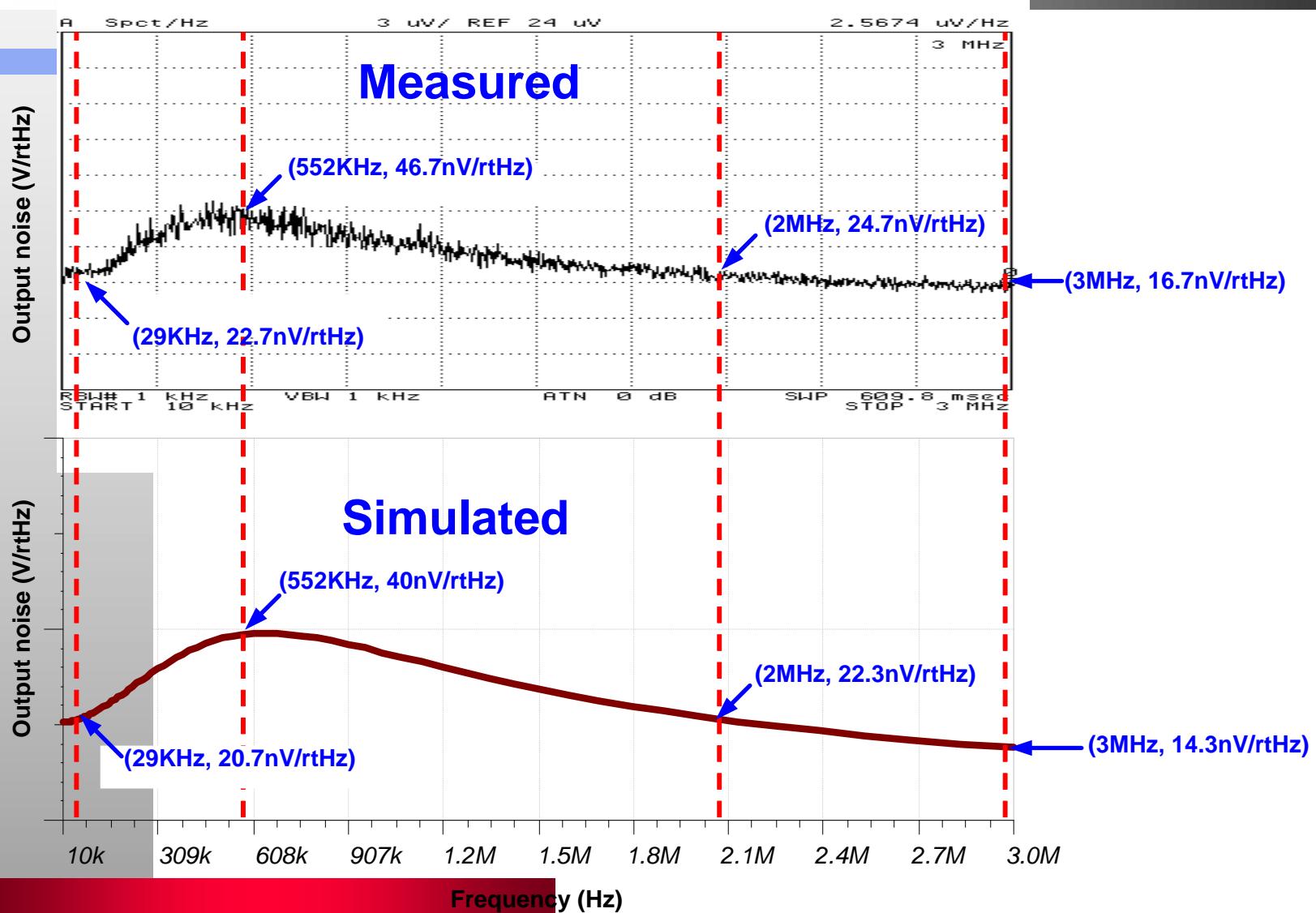OPA827-Noise Density 4395A Spectrum Analyzer



Thank you Gen-Probe Staff

- Nick Nickols (AKA S.E Nickols)
- Science.dmr@gmail.com
- 925-256-0161

References

http://www.radio-electronics.com/info/data/semicond/photo_diode/structures-materials.php

<http://www.rp-photonics.com/photodiodes.html>

<http://www.rp-photonics.com/photodiodes.html>

http://www.radio-electronics.com/info/data/semicond/photo_diode/structures-materials.php

<http://home.sandiego.edu/~ekim/photodiode/pdtech.html>

<http://sales.hamamatsu.com/assets/html/ssd/si-photodiode/index.htm>

Appendix

http://www.radio-electronics.com/info/data/semicond/photo_diode/structures-materials.php

<http://www.rp-photonics.com/photodiodes.html>

<http://www.rp-photonics.com/photodiodes.html>

http://www.radio-electronics.com/info/data/semicond/photo_diode/structures-materials.php

<http://home.sandiego.edu/~ekim/photodiode/pdtech.html>

<http://sales.hamamatsu.com/assets/html/ssd/si-photodiode/index.htm>



Low-Noise, High-Precision, JFET-Input OPERATIONAL AMPLIFIER

FEATURES

- INPUT VOLTAGE NOISE DENSITY: $4\text{nV}/\sqrt{\text{Hz}}$ at 1kHz
- INPUT VOLTAGE NOISE: 0.1Hz to 10Hz: 250nV_{PP}
- INPUT BIAS CURRENT: 15pA
- INPUT OFFSET VOLTAGE: $150\mu\text{V}$ (max)
- INPUT OFFSET DRIFT: $1.5\mu\text{V}/^{\circ}\text{C}$
- GAIN BANDWIDTH: 22MHz
- SLEW RATE: $28\text{V}/\mu\text{s}$
- QUIESCENT CURRENT: $4.8\text{mA}/\text{Ch}$
- WIDE SUPPLY RANGE: $\pm 4\text{V}$ to $\pm 18\text{V}$
- PACKAGES: SO-8 and MSOP-8

APPLICATIONS



- ADC DRIVERS
- DAC OUTPUT BUFFERS
- TEST EQUIPMENT
- MEDICAL EQUIPMENT
- PLL FILTERS
- SEISMIC APPLICATIONS
- TRANSIMPEDANCE AMPLIFIERS
- INTEGRATORS
- ACTIVE FILTERS

DESCRIPTION

The OPA827 series of JFET operational amplifiers combine outstanding dc precision with excellent ac performance. These amplifiers offer low offset voltage ($150\mu\text{V}$, max), very low drift over temperature ($1.5\mu\text{V}/^{\circ}\text{C}$, typ), low bias current (15pA , typ), and very low 0.1Hz to 10Hz noise (250nV_{PP} , typ). The device operates over a wide supply voltage range, $\pm 4\text{V}$ to $\pm 18\text{V}$ on a low supply current ($4.8\text{mA}/\text{Ch}$, typ).

Excellent ac characteristics, such as a 22MHz gain bandwidth product (GBW), a slew rate of $28\text{V}/\mu\text{s}$, and precision dc characteristics make the OPA827 series well-suited for a wide range of applications including 16-bit to 18-bit mixed signal systems, transimpedance (I/V-conversion) amplifiers, filters, precision $\pm 10\text{V}$ front ends, and professional audio applications.

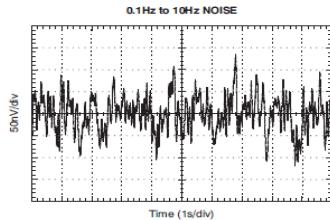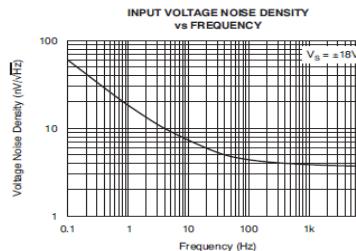The OPA827 is available in both SO-8 and MSOP-8 surface-mount packages, and is specified from -40°C to $+125^{\circ}\text{C}$.



Please be aware that an important notice concerning availability, standard warranty, and use in critical applications of Texas Instruments semiconductor products and disclaimers thereto appears at the end of this data sheet.
All trademarks are the property of their respective owners.

Photodiodes Technologies

•Types of photodiodes:

•Although the term photodiode is widely used, there are actually a number of different types of photodiode technologies that can be used.

PIN photodiode: This type of photodiode is one of the most widely used forms of photodiode today. Although the PIN or p-i-n photodiode was not the first type of photodiode to be used, it collects the light photons more efficiently than the more standard PN photodiode, and also offers a lower capacitance.(Lot's of application and manufacturers)

PN photodiode: The PN photodiode was the first form of photodiode to be developed and used. It is not as widely used as other types which are able to offer better performance parameters. (Solar Cells)

Avalanche photodiode: Avalanche photodiode technology is used in areas of low light. The avalanche photodiode offers very high levels of gain, but against this it has high levels of noise. (Laser range finders)

Schottky photodiode: As the name indicates, Schottky photodiode technology is based upon the Schottky diode. In view of the small diode capacitance it offers a very high speed capability and is used in high bandwidth communication systems.(Telecom/Fiber optics)